

CSC 258 after midterm

JoJo

进度review

Mar 6 – 10	Architecture & microprogramming	Lab 6
Mar 13 – 17	Assembly language basics	Lab 7 & Project proposal
Mar 20 – 24	Assembly language program design	Project demo #1
Mar 27 – 31	Advanced assembly language	Project demo #2
Apr 3 – 5	Topic overflow & course review	Project demo #3 & project report


- ALU – process data
- Storage - Store data
- Control unit – FSM to control the process

LAB 6

- FSM


- $Ax^2 + Bx + C$

Review Before midterm...

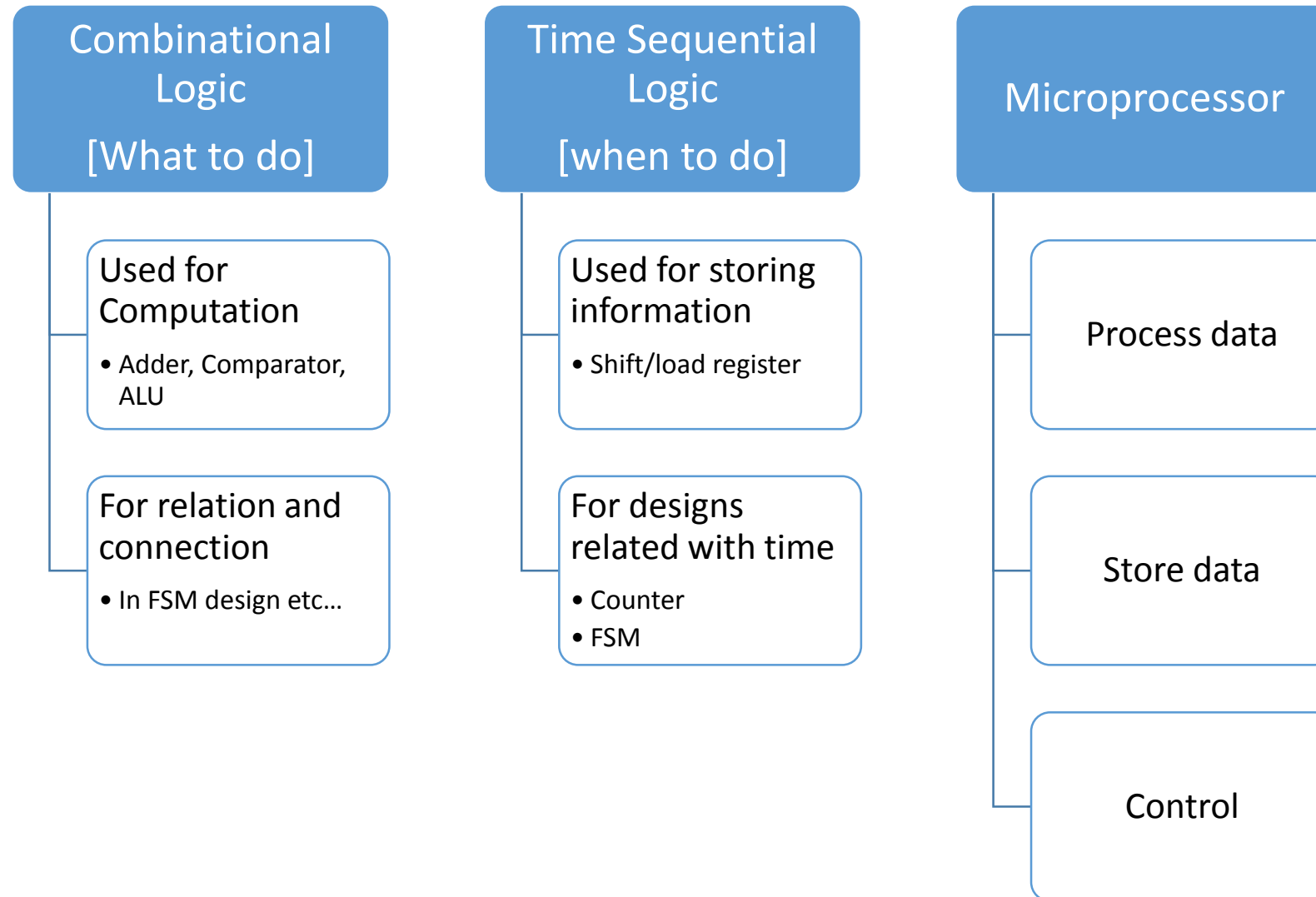

Microprocessor

 - **Defn:** A microprocessor is a computer processor which incorporates the functions of a computer's central processing unit (CPU) on a single integrated circuit (IC), or at most a few integrated circuits.



ALU(Arithmetic Logic Unit)

- What we have before: (一些分立的计算机器)

- Basic Logic computation :
AND/OR/NOT/... GATES
- Basic math computation :
adder/subtractor (multiplication and divide ???)
- Basic comparison


- What we want: (一个完整的计算器)
 - A integrated Computation Block that can handle all

- What we have before:

- module and(a, b, y)
- module or(a, b, y)
- module adder(c_in, a, b, c_out)

- What we want:

 - module (A, B, C_in, Sel, V, C, N, Z, G)
-



ALU(Arithmetic Logic Unit)



- **V**: Overflow condition

- The result of the operation could not be stored in the n bits of G , meaning that the result is incorrect.

- **C**: Carry-out bit

- **N**: Negative indicator

- **Z**: Zero-condition indicator

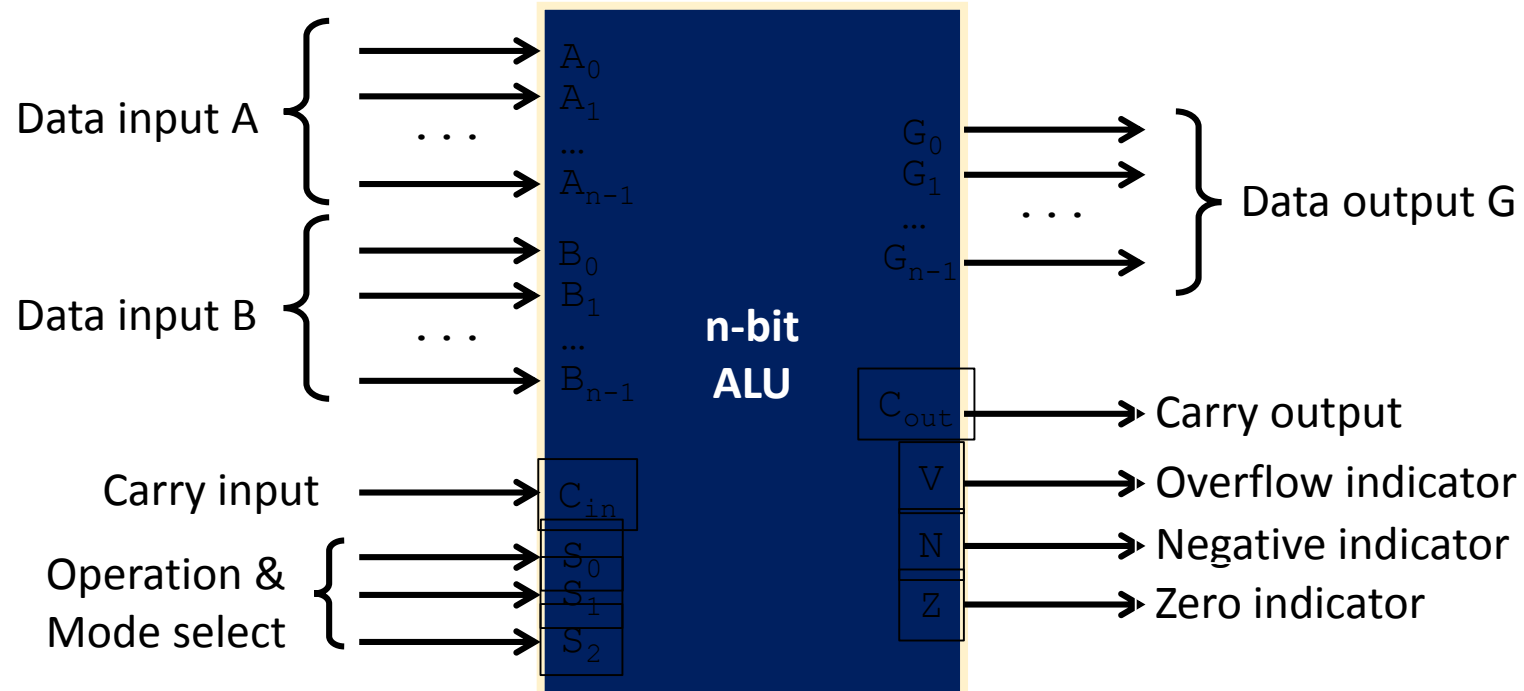 

ALU(Arithmetic Logic Unit)

Select		Input	Operation	
S_1	S_0	Y	$C_{in}=0$	$C_{in}=1$
0	0	All 0s	$G = A$ (transfer)	$G = A+1$ (increment)
0	1	B	$G = A+B$ (add)	$G = A+B+1$
1	0	B	$G = A+B$	$G = A+B+1$ (subtract)
1	1	All 1s	$G = A-1$ (decrement)	$G = A$ (transfer)




- If $S_2 = 1$, then logic circuit block is activated, the combination of S_1 and S_0 can be use SEL signal to choose logic computation like AND, OR, NOR, NOT (up to 4)
- What device should we use here to determine which computation goes to output? A, MUX; B, FSM; C, Decoder; D, Sorting Hat

Shifters and Rotators




- **Shifters** and **rotators** move bits and multiply or divide by powers of 2.
- **Logical shifter** — shifts the number to the left (LSL) or right (LSR) and fills empty spots with 0's.
 - Ex: 11001 LSR 2 00110; 11001 LSL 2 00100
- **Arithmetic shifter**—is the same as a logical shifter, but on right shifts fills the most significant bits with a copy of the old most significant bit (msb).
 - Ex: 11001 ASR 2 11110; 11001 ASL 2 00100
- **Rotator**—rotates number in circle such that empty spots are filled with bits shifted off the other end.
 - Ex: 11001 ROR 2 01110; 11001 ROL 2 00111
- **Special Case(Multiplication)** : $000011(2) \ll 4 = 110000(2) \Leftrightarrow 3(10) * 2^4 = 48(10)$
- **Division: shift to** _____ ?

Shifters and Rotators


- shamt[1:0] means **shift amount**

   

  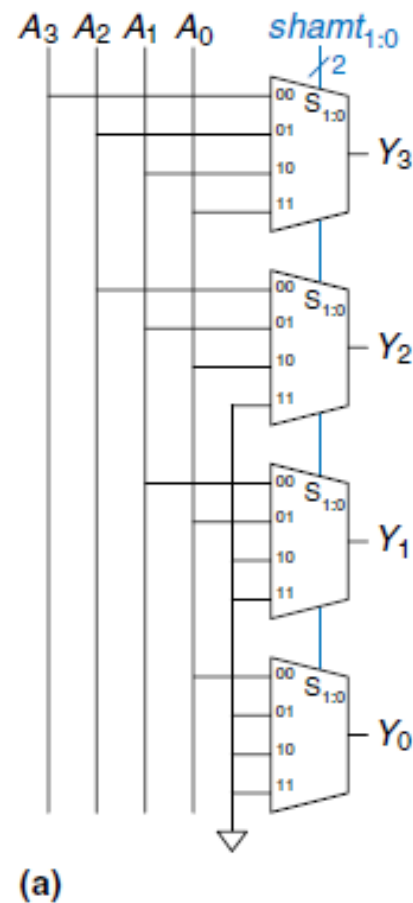- (a) shift left (<<)
- (b) logical shift right (>>)
- (c) arithmetic shift right (>>>)
- 思考题: draw a 4 bit rotator (left / right)



The Final Destination

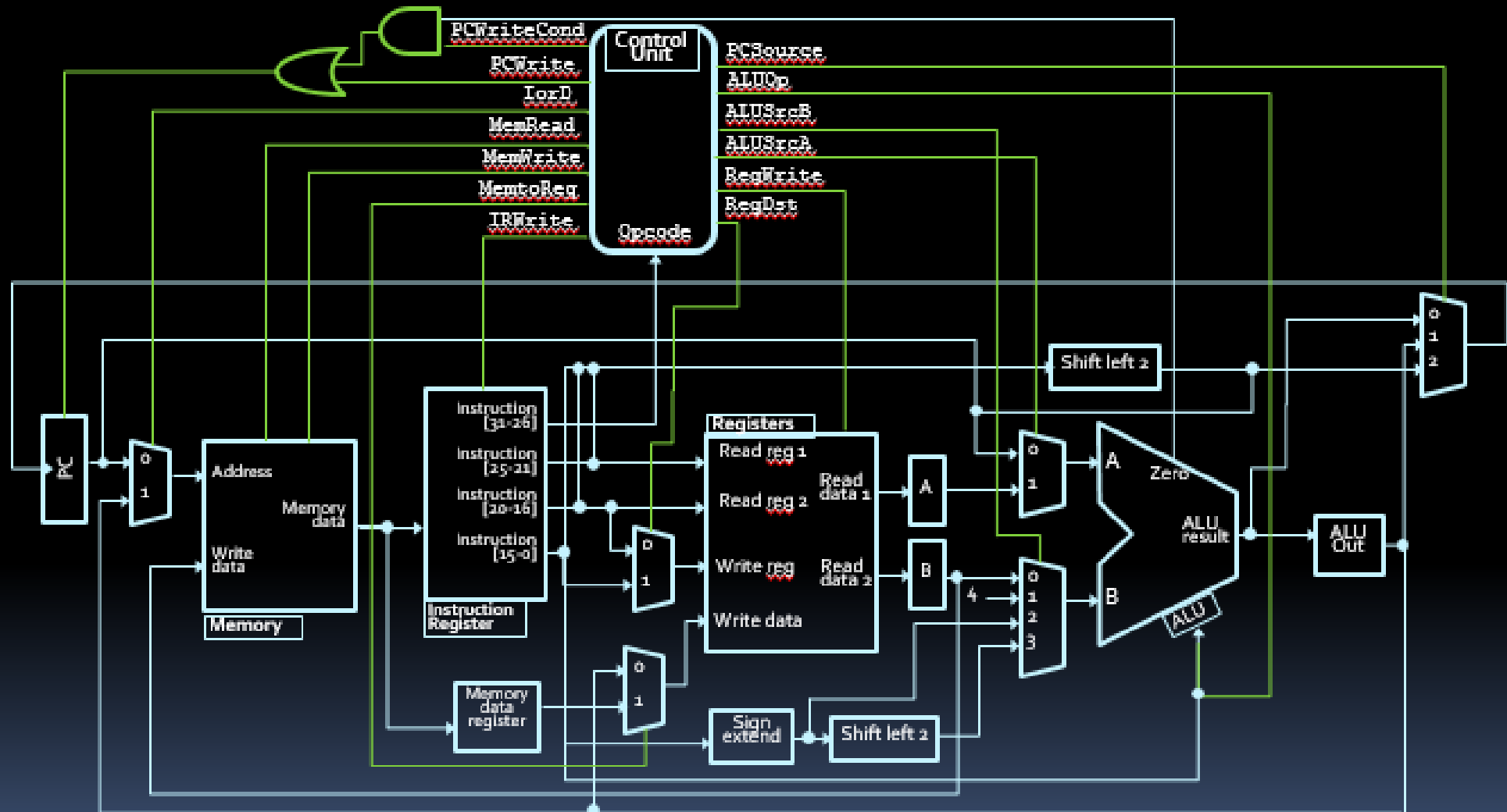

Multiplication (accumulator)


- We want to implement multiplication by **loop**.
- In (i_th) loop
 - if $Y(i) = 1$, we will shift (i - 1) bit X and add the previous result.

230	multiplicand
$\times 42$	multiplier
<hr/>	
460	partial
+ 920	products
<hr/>	
9660	
	result

230 \times 42 = 9660

0101
$\times 0111$
<hr/>
0101
0101
0101
+ 0000
<hr/>
0100011

5 \times 7 = 35

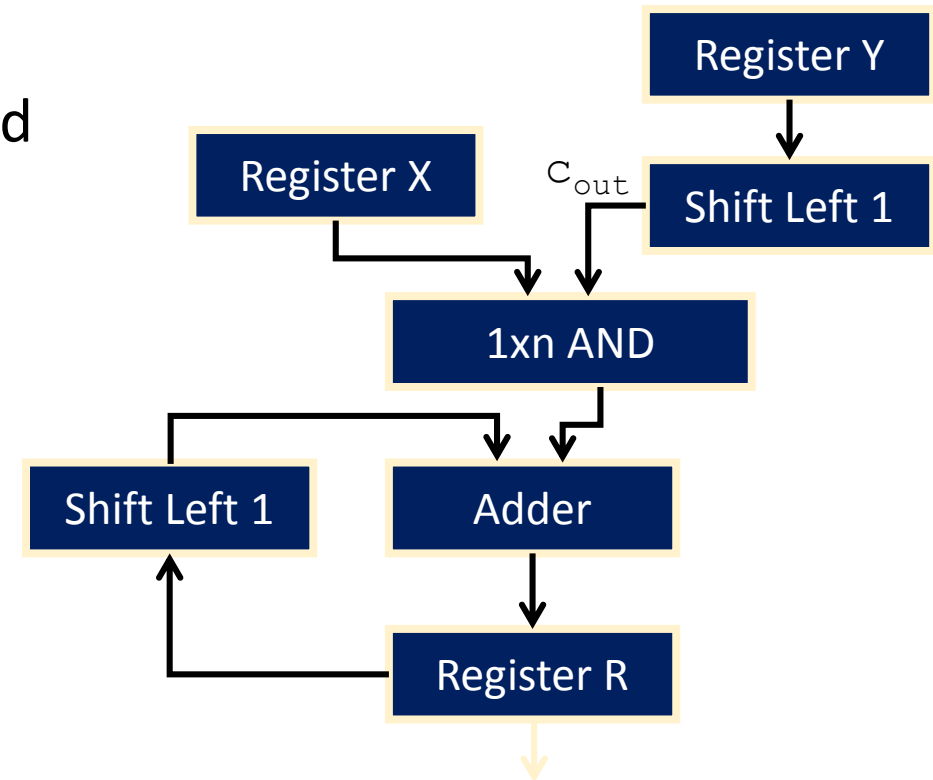

Example

- $M * 0011\ 1110 = M*(2^5 + 2^4 + 2^3 + 2^2 + 2^1) = M * 62$
- Complexity: Shift 5 times and add 5 times;
- If $M*(2^{10} - 1)$
 - Shift ? times and add ? times
- How to reduce the algorithm complexity?
 - $M * 9999 = M*(9*10^4 + 9*10^3 + 9*10^2 + 9*10^1) = M*(10000 - 1)$
 $= M*10^5 - M*1$

Booth algorithm

- 将乘法（分别按位求和，add次数：N-1）根据（01）和（10）的位置转换为纯粹的shift 以及 少量的求和（add次数：n）
- $M * 0011\ 1110 = M * (0100\ 0000 - 0000\ 0010)$
$$= M * (2^6 - 2^1) = M * 62$$
- 事实上，任何二进制数中连续的1可以被分解为两个二进制数之差：
- $0000\ 1111\ 0000 = 0001\ 0000\ 0000 - 0000\ 0001\ 0000;$
- 因此，我们可以用更简单的运算来替换原数中连续为1的数字的乘法，通过加上乘数，对部分积进行移位运算，最后再将之从乘数中减去

Example

- $M * 00111010 = M*(2^5 + 2^4 + 2^3 + 2^1) = M*58$
 $= M*(2^6 - 2^3 + 2^1)$
- Booth Algorithm在遇到一串数字中的第一组从0到1的变化时（即遇到01时）执行加法
- 在遇到这一串连续1的尾部时（即遇到10时）执行减法。
- 这在乘数为负时同样有效。当乘数中的连续1比较多时（形成比较长的1串时），布斯算法较一般的乘法算法执行的加减法运算少。

Step by Step

- 例子参考 Example : $(-5) * 2 = (-10)$
 - (1) $A = 11011$, $B = 00010$, $P = 00000\ 00000$,
 - (2) Add an extra zero bit to the right-most side of A: $A = 110110$
- Repeat $\text{length}(\text{original}(A))$ times:
 - Last 2 digits of A = '10' \rightarrow subtract B from MSB of P $\rightarrow P = 11110\ 00000$ and Arithmetic shift P and A one bit to the right: $A = 111011$, $P = 11111\ 00000$
 - Last 2 digits of A = '11' or '00' \rightarrow do nothing and Arithmetic shift P and A one bit to the right: $A = 111101$, $P = 11111\ 10000$
 - Last 2 digits of A = '01' \rightarrow add B to the MSB of P $\rightarrow P = 00001\ 10000$, and Arithmetic shift P and A one bit to the right: $A = 111110$, $P = 00000\ 11000$
 - keep repeating until reach length of original bit long of $A = 5$;
 - Get final $P = 11111\ 10110 = -10$

12fall final 考题 (by Steve Engels)

- In the space below, perform Booth's Algorithm on the binary values $A=10110$ and $B=01101$. Show your steps in the space provided. **(6 marks)**
- **Solution:**
- **Step (0)** $P = 00000\ 00000$, $A = 10110\ 0$, $-B = 10011$
- Entering the loop (for $i = [1 : \text{length}(\text{original}(A))]$)
- **Step (i = 1):** Last 2 digits of $A = '11'$ or $'00'$ \rightarrow do nothing and Arithmetic shift P and A one bit to the right: $A = 110110$, $P = 00000\ 00000$
- **Step (i = 2):** Last 2 digits of $A = '10'$ \rightarrow subtract B from MSB of $P \rightarrow P = 10011\ 00000$ and Arithmetic shift P and A one bit to the right: $\rightarrow P = 11001\ 10000$, $A = 111011$;
- **Step (i = 3):** similar with $i = 1$ case, Arithmetic shift P and A one bit to the right: $A = 111101$, $P = 11100\ 11000$;
- **Step (i = 4):** Last 2 digits of $A = '01'$ \rightarrow add B to the MSB of $P \rightarrow P = 01001\ 11000$, and Arithmetic shift P and A one bit to the right: $A = 111110$, $P = 00100\ 11100$;
- **Step (i = 5):** same with $(i = 2)$, subtract $\rightarrow P = 10111\ 11100$ and arithmetic shift to right: \rightarrow **$P = 11011\ 11110$**
- **Final $P = 11011\ 11110$.**