 


Logical Devices

We are here



Building up from gates...


- Some common and more complex structures:
 - Multiplexers (MUX)
 - Decoders
 - Seven-segment decoders
 - Adders (half and full)
 - Subtractors
 - Comparators

These are all
Combinational
Circuits

Combinational Circuits

- *Combinational Circuits* are any circuits where the outputs rely strictly on the inputs.
 - Everything we've done so far and what we'll do today is all combinational logic.
- Another category is *sequential circuits* that we will learn in the next weeks.

More Karnaugh Maps

 

Karnaugh map review

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1

- K-maps provide an illustration of a circuit's minterms (or maxterms), and a guide to how neighbouring terms may be combined.

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$

Karnaugh map review

	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	0	1	0
A	1	0	1	1

- K-maps provide an illustration of a circuit's minterms (or maxterms), and a guide to how neighbouring terms may be combined.

$$Y = \bar{A} \cdot B \cdot C + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot \bar{C} + A \cdot B \cdot C$$

$$= B \cdot C + A \cdot \bar{C}$$

Reminder on Reducing Circuits

- Eliminating variables in K-Maps by drawing larger (>1 elements) rectangles results in a circuit with a lower cost function.
- The resulting expression is still in sum-of-products form.
 - But, if simplified, it is *no longer in sum-of-minterms form*.
- Note:** It is not only the number of gates that matters when reducing circuits, but also the number of inputs to each gate.

Karnaugh map example

- Create a circuit with four inputs (A, B, C, D), and two outputs (X, Y):

- The output X is high whenever two or more of the inputs are high.
- The output Y is high when three or more of the inputs are high.

A	B	C	D	X	Y
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1	0	0		
0	1	0	1		
0	1	1	0		
0	1	1	1		
1	0	0	0		
1	0	0	1		
1	0	1	0		
1	0	1	1		
1	1	0	0		
1	1	0	1		
1	1	1	0		
1	1	1	1		

Karnaugh map example

- Create a circuit with four inputs (A, B, C, D), and two outputs (X, Y):

- The output X is high whenever two or more of the inputs are high.
- The output Y is high when three or more of the inputs are high.

A	B	C	D	X	Y
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	0	0
0	0	1	1	1	0
0	1	0	0	0	0
0	1	0	1	1	0
0	1	1	0	1	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	1	0
1	0	1	0	1	0
1	0	1	1	1	1
1	1	0	0	1	0
1	1	0	1	1	1
1	1	1	0	1	1
1	1	1	1	1	1

Karnaugh map example

X:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	1	0
$\bar{A} \cdot B$	0	1	1	1
$A \cdot B$	1	1	1	1
$A \cdot \bar{B}$	0	1	1	1

X =

Karnaugh map example

X:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	1	0
$\bar{A} \cdot B$	0	1	1	1
$A \cdot B$	1	1	1	1
$A \cdot \bar{B}$	0	1	1	1

X = $A \cdot B + C \cdot D + B \cdot D + B \cdot C + A \cdot D + A \cdot C$

Karnaugh map example

Y:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	0	0	0	0
$\bar{A} \cdot B$	0	0	1	0
$A \cdot B$	0	1	1	1
$A \cdot \bar{B}$	0	0	1	0

$$Y = A \cdot B \cdot D + B \cdot C \cdot D + A \cdot B \cdot C + A \cdot C \cdot D$$

Alternative for X: Maxterms

X:

	$C+D$	$C+\bar{D}$	$\bar{C}+\bar{D}$	$\bar{C}+D$
$A+B$	0	0	1	0
$A+\bar{B}$	0	1	1	1
$\bar{A}+\bar{B}$	1	1	1	1
$\bar{A}+B$	0	1	1	1

$$X =$$

Alternative for X: Maxterms

X:

	$C+D$	$C+\bar{D}$	$\bar{C}+\bar{D}$	$\bar{C}+D$
$A+B$	0	0	1	0
$A+\bar{B}$	0	1	1	1
$\bar{A}+\bar{B}$	1	1	1	1
$\bar{A}+B$	0	1	1	1

$$X = (A+C+D) \cdot (B+C+D) \cdot (A+B+C) \cdot (A+B+D)$$

Karnaugh map review


- Note: There are cases where no combinations are possible. K-maps cannot help in these cases.
- Example: Multi-input XOR gates.
 - Output is 1 iff odd number of inputs is 1.



	$\bar{B} \cdot \bar{C}$	$\bar{B} \cdot C$	$B \cdot C$	$B \cdot \bar{C}$
\bar{A}	0	1	0	1
A	1	0	1	0


$$Y = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C$$

Multiplexers

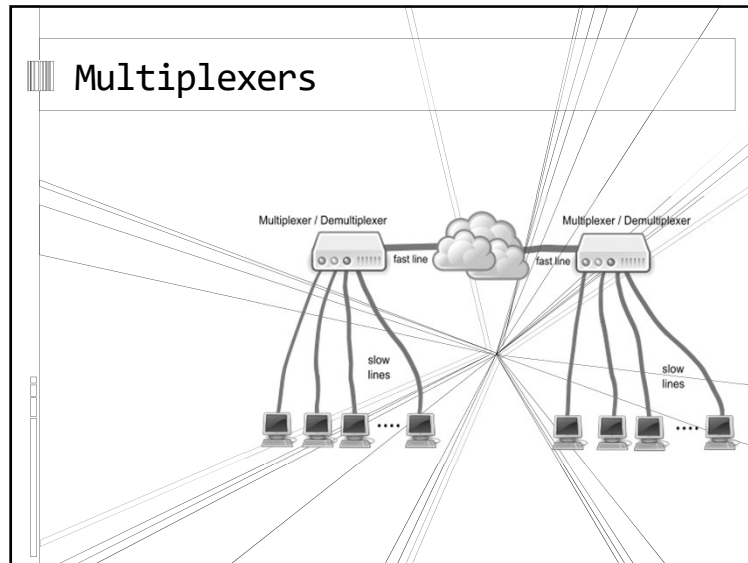

Logic devices

 - Certain structures are common to many circuits, and have block elements of their own.
 - e.g., Multiplexers (short form: mux)
 - **Behaviour:** Output is X if S is 0, and Y if S is 1:
 - S is the select input; X and Y are the data inputs.




Multiplexer design

X	Y	S	M
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

	$\bar{Y} \cdot \bar{S}$	$\bar{Y} \cdot S$	$Y \cdot S$	$Y \cdot \bar{S}$
\bar{X}	0	0	1	0
X	1	0	1	1

$$M = Y \cdot S + X \cdot \bar{S}$$

 

Multiplexers in Verilog

- A four-input multiplexer, created with gates.
 - Note that four input lines require two select bits to choose the output.

```

module mux_gates( select, d, q );
    input[1:0] select;
    input[3:0] d;
    output    q;

    wire      q, q1, q2, q3, q4;
    wire      not_s0, not_s1;
    wire[1:0] select;
    wire[3:0] d;

    not n1( not_s0, select[0] );
    not n2( not_s1, select[1] );

    and a1( q1, not_s0, not_s1, d[0] );
    and a2( q2, select[0], not_s1, d[1] );
    and a3( q3, not_s0, select[1], d[2] );
    and a4( q4, select[0], select[1], d[3] );

    or o1( q, q1, q2, q3, q4 );

endmodule
    
```

Multiplexers in Verilog

- Another four-input mux, this time implemented using boolean notation

```
module mux_logic( select, d, q );
```

```
input[1:0] select;
input[3:0] d;
output q;
```

```
wire q;
wire[1:0] select;
wire[3:0] d;
```

```
assign q = (~select[1]&~select[0] &d[0] |
            (~select[1]&select[0] &d[1] |
            (select[1]&~select[0] &d[2] |
            (select[1]&select[0] &d[3]);
```

```
endmodule
```

specify input

specify value

In Lab2 you need to implement a 4-to-1 mux differently, using hierarchical design.



Multiplexer uses

- Muxes are very useful whenever you need to select from multiple input values.
 - Example: surveillance video monitors, digital cable boxes, routers.




Demultiplexers

  - Related to decoders: demultiplexers.
 - Does multiplexer operation, in reverse.



Mux + Demux

 


Source:
https://upload.wikimedia.org/wikipedia/commons/e/eo/Telephony_multiplexer_system.gif

Decoders



Decoders

 
- Decoders are essentially translators.
 - Translate from the output of one circuit to the input of another.
 - Think of them as providing a mapping between 2 different encodings!
- Example: Binary signal splitter
 - Activates one of four output lines, based on a two-digit binary number.




7-segment decoder



 - Common and useful decoder application.
 - Translate from a 4-digit binary number to the seven segments of a digital display.
 - Each output segment has a particular logic that defines it.
 - Example: Segment 0
 - Activate for values: 0, 2, 3, 5, 6, 7, 8, 9.
 - In binary: 0000, 0010, 0011, 0101, 0110, 0111, 1000, 1001.
 - First step: Build the truth table and K-map.



7-segment decoder

 


- For 7-seg decoders, turning a segment on involves driving it low.
- Example: Displaying digits 0-9
 - Assume input is a 4-digit binary number
 - Segment 0 (top segment) is low whenever the input values are 0000, 0010, 0011, 0101, 0110, 0111, 1000 or 1001, and high whenever input number is 0001 or 0100.
 - This create a truth table and map like the following...

7-segment decoder

x_3	x_2	x_1	x_0	HEX ₀
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

 - HEX₀ = $\bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0$
+ $\bar{x}_3 \cdot x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$
- But wait...what about input values 1010 to 1111?



“Don’t care” values

- Input values that will never happen or are not meaningful in a given design, and so their output values do not have to be defined.
 - Recorded as 'x' in truth-tables and K-Maps.
- In the K-maps we can think of these don't care values as either 0 or 1 depending on what helps us simplify our circuit.
 - Note you do NOT change the X with a 0 or 1, you just include it in a grouping as needed.

“Don’t care” values

- New equation for HEX₀:

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	1	0	0
$\bar{x}_3 \cdot x_2$	1	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x

$$\text{HEX}_0 = \bar{x}_3 \cdot \bar{x}_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot \bar{x}_1 \cdot \bar{x}_0$$

Again for segment 1

x_3	x_2	x_1	x_0	HEX ₁
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	0
$\bar{x}_3 \cdot x_2$	0	1	0	1
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x


$$\text{HEX}_1 = x_2 \cdot \bar{x}_1 \cdot x_0 + x_2 \cdot x_1 \cdot \bar{x}_0$$

Again for segment 2

x_3	x_2	x_1	x_0	HEX ₂
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0

	$\bar{x}_1 \cdot \bar{x}_0$	$\bar{x}_1 \cdot x_0$	$x_1 \cdot x_0$	$x_1 \cdot \bar{x}_0$
$\bar{x}_3 \cdot \bar{x}_2$	0	0	0	1
$\bar{x}_3 \cdot x_2$	0	0	0	0
$x_3 \cdot x_2$	x	x	x	x
$x_3 \cdot \bar{x}_2$	0	0	x	x
 
$$\text{HEX2} = \bar{x}_2 \cdot x_1 \cdot \bar{x}_0$$



Verilog for 7-segment display


```
//Seven segment decoder for BCD inputs from 0 to 9
module seven_seg_decoder(S,HEX0);

input [3:0]S;
output [6:0]HEX0;

assign HEX0[0]=(~S[3]&~S[2]&~S[1]&S[0])|(S[2]&~S[1]&~S[0]);
assign HEX0[1]=(S[2]&~S[1]&S[0])|(S[2]&S[1]&~S[0]);
assign HEX0[2]=~S[2]&S[1]&~S[0];
... // remaining equations left as an exercise
endmodule
```

The final 7-seg decoder

 - Decoders all look the same, except for the inputs and outputs.
- Unlike other devices, the implementation differs from decoder to decoder.



Another “don’t care” example

(not related to decoders)


- Climate control fan:
 - The fan should turn on (F) if the temperature is hot (H) or if the temperature is cold (C), depending on whether the unit is set to A/C or heating (A).

H	C	A	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

	$\bar{H} \cdot \bar{C}$	$\bar{H} \cdot C$	$H \cdot C$	$H \cdot \bar{C}$
\bar{A}	0	1	x	0
A	0	0	x	1

$$F = A \cdot H + \bar{A} \cdot C$$

Adder circuits

 

Adders

- Also known as binary adders.
 - Small circuit devices that add two digits together.
 - Combined together to create iterative combinational circuits.
- Types of adders:
 - Half adders (HA)
 - Full adders (FA)
 - Ripple Carry Adder



Review of Binary Math

- Each digit of a decimal number represents a power of 10:

$$258 = 2 \times 10^2 + 5 \times 10^1 + 8 \times 10^0$$

- Each digit of a binary number represents a power of 2:

$$01101_2 = 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 \\ = 13_{10}$$

Decimal to Binary Conversion

- Let's say I give you number 11 in decimal. How would you represent this in binary?

- Keep dividing by 2 and write down the remainders!

Use the quotient from previous row.

Number	Quotient = Number / 2	Remainder = Number % 2	
11			

11 in decimal is 1011 in binary!

Decimal to Binary Conversion

- Let's say I give you number 11 in decimal. How would you represent this in binary?

- Keep dividing by 2 and write down the remainders!

11 in decimal is 1011 in binary!

Use the quotient from previous row.

Number	Quotient = Number / 2	Remainder = Number % 2	
11	5	1	Least Significant Bit
5	2	1	
2	1	0	
1	0	1	Most Significant Bit

Hexadecimal Numbers

- Base 16 numbers, where valid values are:

- 0 to 9 as in decimal, and
- 10 is A
- 11 is B
- ..
- 15 is F

Hex numbers are typically expressed as 0x_____

- Writing a binary number in hex(-adecimal):


- 0000010111111010 = 0000 0101 1111 1010 = 0x05fa
- In Verilog (more about this in the handout of Lab 3):
 - 16'b0000_0101_1111_1010
 - 16'h05FA (16'h05fa is fine too)

Unsigned binary addition

- 27 + 53

27 = 00011011

53 = 00110101

 


Unsigned binary addition

- 27 + 53

27 = 00011011


53 = 00110101

 

- 95 + 181

01011111

+10110101

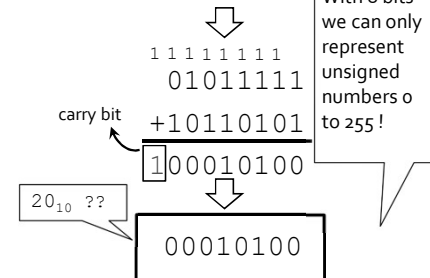


With 8 bits we can only represent unsigned numbers 0 to 255!

Half Adders

- A 2-input, 1-bit width binary adder that performs the following computations:


X	0	0	1	1
+Y	+0	+1	+0	+1
CS	00	01	01	10

 - A half adder adds two bits to produce a two-bit sum.
- The sum is expressed as a sum bit S and a carry bit C.




Half Adder Implementation

 - Equations and circuits for half adder units are easy to define (even without Karnaugh maps)



Half Adder Implementation

 
- Equations and circuits for half adder units are easy to define (even without Karnaugh maps)



Full Adders

- Similar to half-adders, but with another input Z, which represents a carry-in bit.
 - C and Z are sometimes labeled as C_{out} and C_{in} .
- When Z is 0, the unit behaves exactly like a half adder.
- When Z is 1:

X	0	0	1	1
+Y	+0	+1	+0	+1
+Z	+1	+1	+1	+1
CS	01	10	10	11

 

Full Adder Design

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$C = X \cdot Y + X \cdot Z + Y \cdot Z$$

C	$\bar{Y} \cdot \bar{Z}$	$\bar{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \bar{Z}$
\bar{x}	0	0	1	0
x	0	1	1	1

S	$\bar{Y} \cdot \bar{Z}$	$\bar{Y} \cdot Z$	$Y \cdot Z$	$Y \cdot \bar{Z}$
\bar{x}	0	1	0	1
x	1	0	1	0


$$S = X \oplus Y \oplus Z$$

Full Adder Design

- The C term can also be rewritten as:


$$C = X \cdot Y + (X \oplus Y) \cdot Z$$

 - Two terms come from this:
 - $X \cdot Y = \text{carry generate (G)}$.
 - $X \oplus Y = \text{carry propagate (P)}$.
- Results in this circuit →



Ripple-Carry Binary Adder

 - Full adder units are chained together in order to perform operations on signal vectors.



Adders in Verilog

- Verilog code that implements a half adder unit.

```
module half_adder (in_x, in_y, out_sum, out_carry);
    input  in_x;
    input  in_y;
    output out_sum;
    output out_carry;

    assign out_sum = in_x^in_y;
    assign out_carry = in_x&in_y;

endmodule
```

Adders in Verilog

- Verilog code that implements a full adder unit.

```
module full_adder(sum,cout,a,b,cin);  
    output sum, cout;  
    input a, b, cin;  
  
    assign sum = a^b^cin;  
    assign cout = (a&b)|(cin&(a^b));  
  
endmodule
```

```
module full_adder(sum,cout,a,b,cin);  
    output sum, cout;  
    input a,b,cin;  
  
    assign {cout,sum}=a+b+cin;  
  
endmodule
```

The role of C_{in}

- Why can't we just have a half-adder for the smallest (right-most) bit?
- We could, if we were only interested in addition. But the last bit allows us to do subtraction as well!
 - Time for a little fun with subtraction!

Fun with Subtraction

- Find a partner.
- Have each person choose a five-digit binary number.
- Take the smaller number, and invert all the digits.
- Add this inverted number to the larger one.
- Add one to the result.
- Check what the result is...



Subtractors

- Subtractors are an extension of adders.
 - Basically, perform addition on a negative number.
- Before we can do subtraction, need to understand negative binary numbers.
- Two types:
 - Unsigned = a separate bit exists for the sign; data bits store the positive version of the number.
 - Signed = all bits are used to store a 2's complement negative number.
 - More common, and what we use for this course.

Two's complement

- Need to know how to get 1's complement:
 - Given number X with n bits, take $(2^n - 1) - X$
 - Negates each individual bit (bitwise NOT).

01001101	→	10110010
11111111	→	00000000

- 2's complement = (1's complement + 1) } Know this!

01001101	→	10110011
11111111	→	00000001

- Note:** Adding a 2's complement number to the original number produces a result of zero.

Signed subtraction

- Negative numbers are generally stored in 2's complement notation.
 - Reminder:** 1's complement → bits are the bitwise NOT of the equivalent positive value.
 - 2's complement → one more than 1's complement value; results in zero when added to equivalent positive value.
 - Subtraction can then be performed by using the binary adder circuit with negative numbers.

Signed representations

Decimal	Unsigned	Signed 2's
7	111	---
6	110	---
5	101	---
4	100	---
3	011	011
2	010	010
1	001	001
0	000	000
-1	---	111
-2	---	110
-3	---	101
-4	---	100

Rules about signed numbers

- When thinking of signed binary numbers, there are a few useful rules to remember:
 - The largest positive binary number is a zero followed by all ones.
 - The binary value for -1 has ones in all the digits.
 - The most negative binary number is a one followed by all zeroes.
- There are 2^n possible values that can be stored in an n -digit binary number.
 - 2^{n-1} are negative, $2^{n-1}-1$ are positive, and one is zero.
 - For example, given an 8-bit binary number:
 - There are 256 possible values
 - One of those values is zero
 - 128 are negative values (11111111 to 10000000)
 - 127 are positive values (00000001 to 01111111)



Practice 2's complement!

- Assume 4-bits signed representation!
- Write these decimal numbers in binary:

2	=> 0010
-1	=> 1111
0	=> 0000
8	=> Not possible to represent!
-8	=> 1000

- What is max positive number? => 7 (i.e., $2^{4-1} - 1$)
- What is min negative number? => -8 (i.e., -2^{4-1})

Subtraction at the core

- Subtraction is nothing more than addition of a negative number
 - $7 - 3 = 7 + (-3)$
 - $-3 - 2 = -3 + (-2)$

Signed Subtraction example

- $7 - 3$

$$\begin{array}{r}
 0111 \\
 -0011 \\
 \hline
 0111 \\
 \downarrow \\
 \text{discarded } +1101 \\
 \begin{array}{r}
 10100 \\
 \hline
 0100 = 4_{10}
 \end{array}
 \end{array}$$

- $-3 - 2$

$$\begin{array}{r}
 1101 \\
 -0010 \\
 \hline
 1101 \\
 \downarrow \\
 \text{discarded } +1110 \\
 \begin{array}{r}
 11011 \\
 \hline
 1011 = -5_{10}
 \end{array}
 \end{array}$$

What about bigger numbers

- $53 - 27$

$$\begin{array}{r}
 00110101 \\
 -00011011 \\
 \hline
 00110101 \\
 \downarrow \\
 \text{discarded } +11100101 \\
 \begin{array}{r}
 100011010 \\
 \hline
 00011010 = 26_{10}
 \end{array}
 \end{array}$$

- $27 - 53$


$$\begin{array}{r}
 00011011 \\
 -00110101 \\
 \hline
 00011011 \\
 \downarrow \\
 \text{discarded } +11001011 \\
 \begin{array}{r}
 011100110 \\
 \hline
 11100110 = -26_{10}
 \end{array}
 \end{array}$$

Subtraction circuit


- 4-bit subtractor: $X - Y$
 - X plus 2's complement of Y
 - X plus 1's complement of Y plus 1

Feed 1 as Carry-In in the least significant FA.

 Use NOT gates to get the 1's complement of Y .



Addition/Subtraction circuit

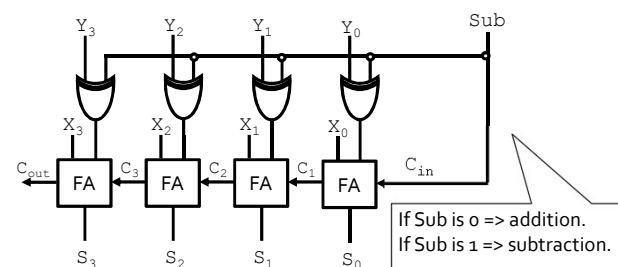

- The full adder circuit can be expanded to incorporate the subtraction operation.
 - Remember:** 2's complement = 1's complement + 1
 - We need Sub fed as Cin

Food for Thought


- What happens if we add these two positive signed binary numbers $0110 + 0011$ (i.e., $6 + 3$)?
 - The result is 1001 .
 - But that is a negative number (-7)! ☹
- What happens if we add the two negative numbers $1000 + 1111$ (i.e., $-8 + (-1)$)?
 - The result is 0111 with a carry-out. ☹
- We need to know when the result might be wrong.
 - This is usually indicated in hardware by the Overflow flag!
 - More about this when we'll talk about processors.

Unsigned subtraction


- Special case: separate sign bit is used.
- General algorithm:
 - Get the 2's complement of the subtrahend (the term being subtracted).
 - Add that value to the minuend (the term being subtracted from).
 - If there is an end carry (C_{out} is high), the final result is positive and does not change.
 - If there is no end carry (C_{out} is low), get the 2's complement of the result and add a negative sign to it (or set the sign bit high).

Unsigned subtraction example

▪ $53 - 27$

 

▪ $27 - 53$

 

Sign & Magnitude Representation

- The Sign part: one bit is designated as the sign (+/-).
 - 0 for positive numbers
 - 1 for negative numbers
- The Magnitude part: Remaining bits store the positive (i.e., unsigned) version of the number.
- Example: 4-bit binary numbers:
 - 0110 is 6 while 1110 is -6 (most significant bit is the sign)
 - What about 0000 and 1000? => zero (two ways)
- Sign-magnitude computation is more complicated.
 - 2's complement is what today's systems use!

Comparators



Comparators

- A circuit that takes in two input vectors, and determines if the first is greater than, less than or equal to the second.
- How does one make that in a circuit?



Basic Comparators

- Consider two binary numbers A and B, where A and B are one bit long.

- The circuits for this would be:

□ $A=B$:


$$A \cdot B + \bar{A} \cdot \bar{B}$$

□ $A>B$:

$$A \cdot \bar{B}$$

□ $A<B$:

$$\bar{A} \cdot B$$

 

A	B
0	0
0	1
1	0
1	1

Basic Comparators


- What if A and B are two bits long?
- The terms for this circuit have to expand to reflect the second signal.
- For example:

□ $A=B$:

$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

Make sure that the values of bit 1 are the same

 Make sure that the values of bit 0 are the same



Basic Comparators

- What about checking if A is greater or less than B?

□ $A>B$:

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$


Check if first bit satisfies condition

If not, check that the first bits are equal...

...and then do the 1-bit comparison

□ $A<B$:
 
$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$



Basic Comparators

- The final circuit equations for two-input comparators are shown below.
- Note the sections they have in common!

□ $A=B$:


$$(A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot B_0 + \bar{A}_0 \cdot \bar{B}_0)$$

□ $A>B$:

$$A_1 \cdot \bar{B}_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (A_0 \cdot \bar{B}_0)$$

□ $A<B$:
 
$$\bar{A}_1 \cdot B_1 + (A_1 \cdot B_1 + \bar{A}_1 \cdot \bar{B}_1) \cdot (\bar{A}_0 \cdot B_0)$$



General Comparators

- The general circuit for comparators requires you to define equations for each case.
- Case #1: Equality**
 - If inputs A and B are equal, then all bits must be the same.
 - Define X_i for any digit i :
 - (equality for digit i)
 - Equality between A and B is defined as:

$$X_i = A_i \cdot B_i + \bar{A}_i \cdot \bar{B}_i$$

$$A=B : X_0 \cdot X_1 \cdot \dots \cdot X_n$$

Comparators

- Case #2: $A > B$**
 - The first non-matching bits occur at bit i , where $A_i=1$ and $B_i=0$. All higher bits match.
 - Using the definition for X_i from before:

$$A > B = A_n \cdot \bar{B}_n + X_n \cdot A_{n-1} \cdot \bar{B}_{n-1} + \dots + A_0 \cdot \bar{B}_0 \cdot \prod_{k=1}^n X_k$$

- Case #3: $A < B$**
 - The first non-matching bits occur at bit i , where $A_i=0$ and $B_i=1$. Again, all higher bits match.

$$A < B = \bar{A}_n \cdot B_n + X_n \cdot \bar{A}_{n-1} \cdot B_{n-1} + \dots + \bar{A}_0 \cdot B_0 \cdot \prod_{k=1}^n X_k$$

Comparator truth table

- Given two input vectors of size $n=2$, output of circuit is shown at right.

Inputs				Outputs		
A_1	A_0	B_1	B_0	$A < B$	$A = B$	$A > B$
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Comparator example (cont'd)

$A < B$:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	1	1	1
$A_0 \cdot \bar{A}_1$	0	0	1	1
$A_0 \cdot A_1$	0	0	0	0
$\bar{A}_0 \cdot A_1$	0	0	1	0

$$LT = B_1 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot \bar{A}_0 + B_0 \cdot \bar{A}_0 \cdot \bar{A}_1$$

Comparator example (cont'd)

A=B:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot \bar{A}_1$	0	1	0	0
$A_0 \cdot A_1$	0	0	1	0
$\bar{A}_0 \cdot A_1$	0	0	0	1

$$EQ = \bar{B}_0 \cdot \bar{B}_1 \cdot \bar{A}_0 \cdot \bar{A}_1 + B_0 \cdot \bar{B}_1 \cdot A_0 \cdot \bar{A}_1 + B_0 \cdot B_1 \cdot A_0 \cdot A_1 + \bar{B}_0 \cdot B_1 \cdot \bar{A}_0 \cdot A_1$$

Comparator example (cont'd)

A>B:

	$\bar{B}_0 \cdot \bar{B}_1$	$B_0 \cdot \bar{B}_1$	$B_0 \cdot B_1$	$\bar{B}_0 \cdot B_1$
$\bar{A}_0 \cdot \bar{A}_1$	0	0	0	0
$A_0 \cdot \bar{A}_1$	1	0	0	0
$A_0 \cdot A_1$	1	1	0	1
$\bar{A}_0 \cdot A_1$	1	1	0	0

$$GT = \bar{B}_1 \cdot A_1 + \bar{B}_0 \cdot \bar{B}_1 \cdot A_0 + \bar{B}_0 \cdot A_0 \cdot A_1$$

Comparators in Verilog

- Implementing a comparator can be done by putting together the circuits as shown in the previous slide, or by using the comparison operators to make things a little easier:

```
module comparator_4_bit (a_gt_b, a_lt_b, a_eq_b, a, b);
    input [3:0] a, b;
    output a_gt_b, a_lt_b, a_eq_b;

    assign a_gt_b = (a > b);
    assign a_lt_b = (a < b);
    assign a_eq_b = (a == b);

endmodule
```

Comparing larger numbers

- As numbers get larger, the comparator circuit gets more complex.
- At a certain level, it can be easier sometimes to just process the result of a subtraction operation instead.
 - Easier, less circuitry, just not faster.

