
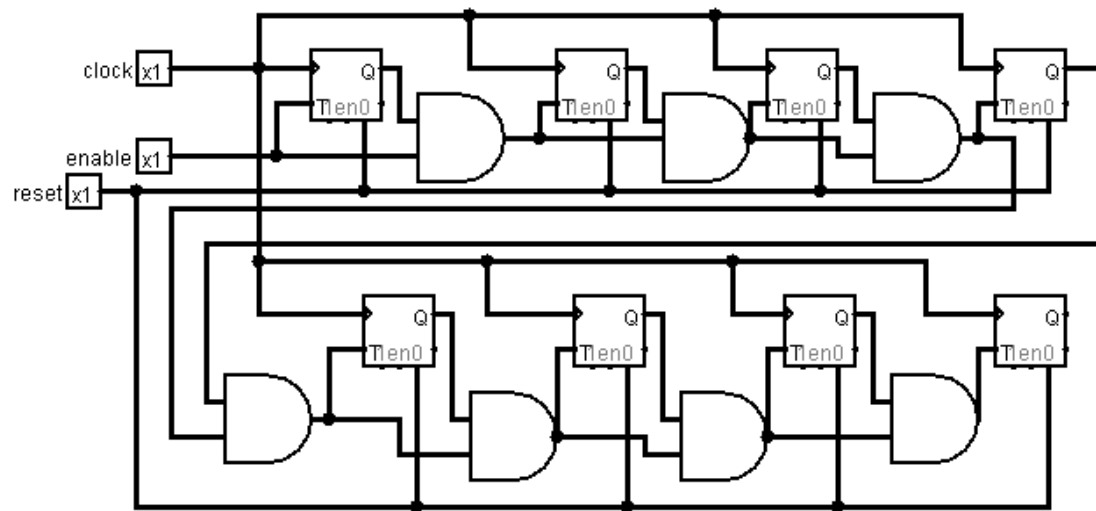


CSC258 Lab5 Prelab

Prart 1 1. schematic

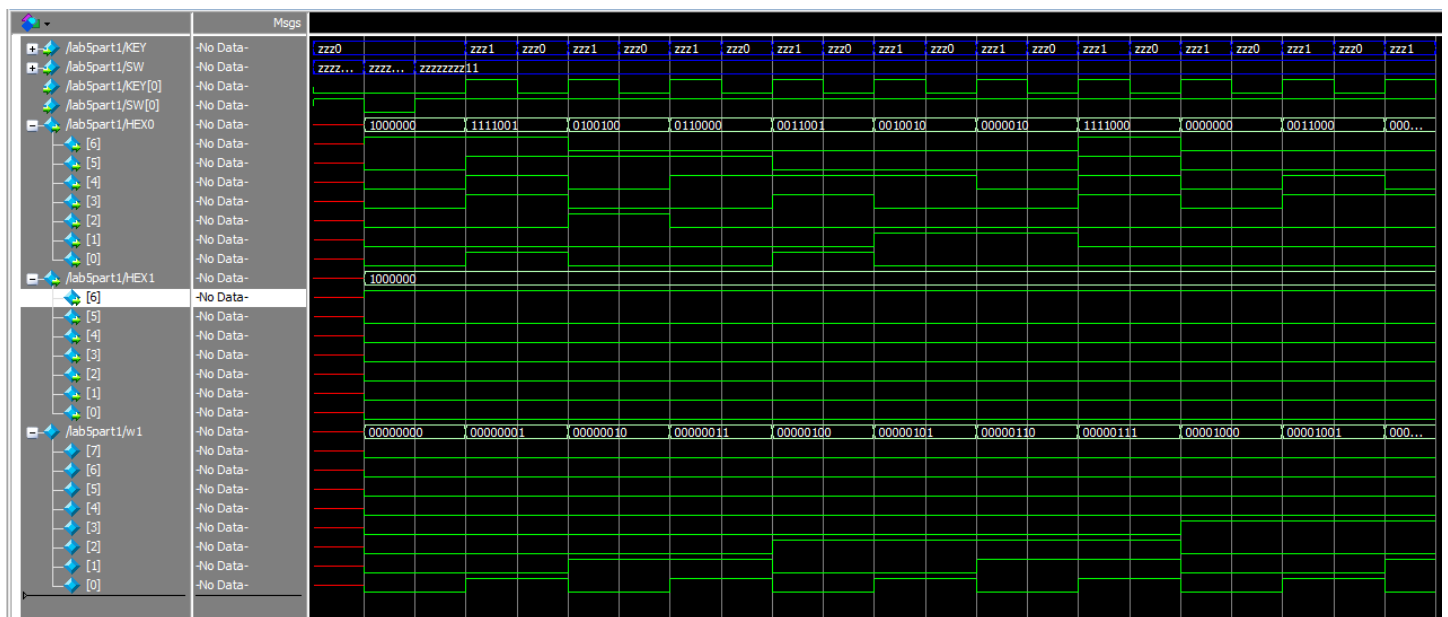

4.



5. a) The Logic utilization (in ALMs) is 14/32,070 (<1%)

b) I cannot find the report. But I guess it is 50MHz.

7. The T flip flop are vertically placed.

Part 2:

0. A counter with $\log_2 50000000 = 26$ to count to 50 million.

1.

