



# Week 3 review

# Announcements

- Mid-term exam for CSC 258:
  - On Friday, 22 June 2018, 2.00 – 4.00pm
  - Last names: A – M at BA2145
  - Last names: O – Z at BA2155
- Class List – sign while submitting in-class exercise
- In-Class Exercise
  - underline your last name
  - write the PS set number (PS 04) or today's date
  - write the course code (CSC 258)
  - sign the PS submission list when submitting your set

# Question #1

- a) How do you write the number 78 as an 8-bit binary number?

128	64	32	16	8	4	2	1
0	1	0	0	1	1	1	0

- b) What is the two's complement of 01101101?

10010011

- c) What is the sum of 01101101 and 01101101?

11011010

← Note what's happening here!

## Question #2


- What groupings are in the K-map on the right?

	$\bar{C} \cdot \bar{D}$	$C \cdot \bar{D}$	$C \cdot D$	$\bar{C} \cdot D$
$\bar{A} \cdot \bar{B}$	1	1	X	1
$A \cdot \bar{B}$	X	0	X	1
$A \cdot B$	1	X	X	1
$\bar{A} \cdot B$	1	X	0	X

- What logic equations do these groupings represent?

$$\bar{A} \cdot \bar{B} + \bar{C}$$

## Question #3

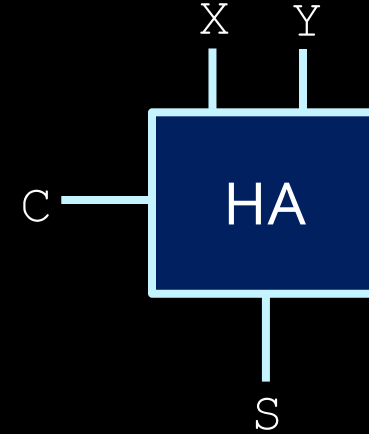

- Implement a half adder in Verilog.
- **Step 1:** What is the half adder logic equation?


$$\begin{aligned} C &= X \cdot Y & S &= X \cdot \bar{Y} + \bar{X} \cdot Y \\ & & &= X \oplus Y \end{aligned}$$

- **Step 2:** Equivalent Verilog components.

```
assign C = X & Y;  
assign S = X & ~Y | ~X & Y;
```
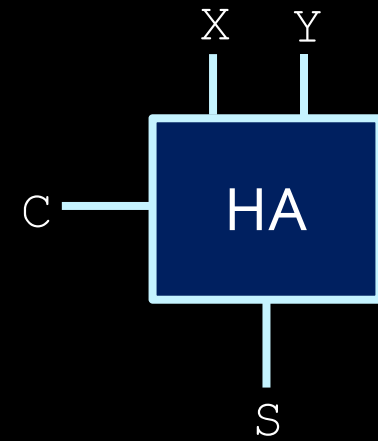
## Question #3 (cont'd)

- **Step 3:** What is the complete Verilog code for this device?




```
module half_adder(X, Y, C, S);  
    input X, Y;  
    output C, S;  
  
    assign C = X & Y;  
    assign S = X & ~Y | ~X & Y;  
endmodule
```



# Problem Set 03

# Question 1

What gate is created by the following?

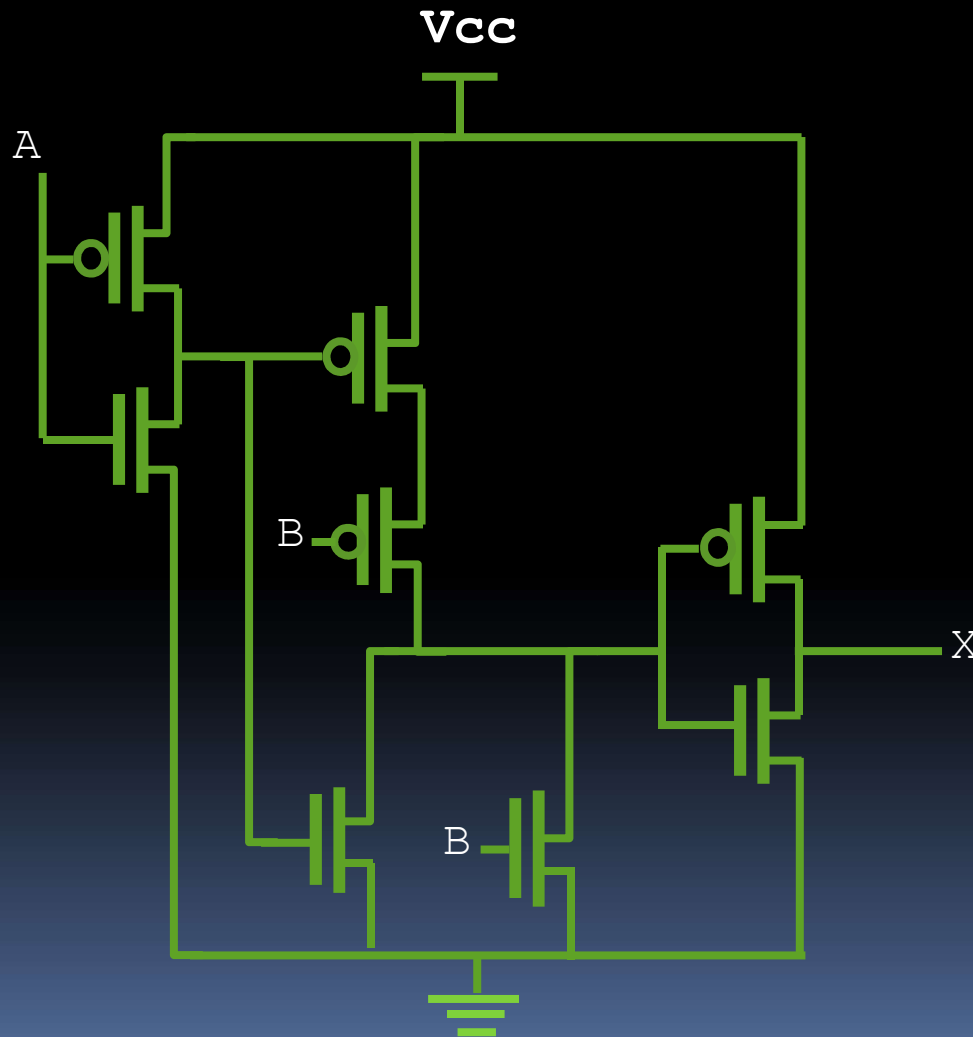

A	B	X
0	0	1
0	1	1
1	0	0
1	1	1

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

$$X = \overline{(\overline{A} \cdot \overline{B})} \quad \text{or}$$

$$X = \overline{A} + B$$



## Question 2 - Minterms

- Write Y in SOM (Sum Of Minterms) form.

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$Y = \bar{A} \cdot \bar{B} \cdot C + \bar{A} \cdot B \cdot \bar{C} + A \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C$$

$$Y = m_1 + m_2 + m_4 + m_7$$

# Question 3

- What is the most reduced form, in sum of products form, of the function from the truth table on the right?

$$Y = m_0 + m_1 + m_2 + m_5 \\ + m_7 + m_8 + m_9 \\ + m_{10} + m_{13} + m_{15}$$

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	1

## Question #4 (cont'd)

	$\overline{C} \cdot \overline{D}$	$\overline{C} \cdot D$	$C \cdot D$	$C \cdot \overline{D}$
$\overline{A} \cdot \overline{B}$	1	1	0	1
$\overline{A} \cdot B$	0	1	1	0
$A \cdot B$	0	1	1	0
$A \cdot \overline{B}$	1	1	0	1

$$Y = \overline{C} \cdot D + B \cdot D + \overline{B} \cdot \overline{D}$$

## Question #4 (alternative)

- An alternative grouping:

	$\bar{C} \cdot \bar{D}$	$\bar{C} \cdot D$	$C \cdot D$	$C \cdot \bar{D}$
$\bar{A} \cdot \bar{B}$	1	1	0	1
$\bar{A} \cdot B$	0	1	1	0
$A \cdot B$	0	1	1	0
$A \cdot \bar{B}$	1	1	0	1

$$Y = \bar{B} \cdot \bar{C} + B \cdot D + \bar{B} \cdot \bar{D}$$



# Problem Set 03

# Questions

1. Convert the following decimal values to 2's complement number:
  - -89
  - -62
2. Convert the following 2's complement number to its decimal equivalent
  - 10110011
  - 10000011
3. Perform binary subtraction on these two numbers: 103 and 69. Show the steps.

## Question 4: Full Adder

x	y	z	c	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Simplify the following two equations so that they use at least one XOR gate ( $\oplus$ ):

$$\begin{aligned}C &= \sum(3,5,6,7) \\&= \\&=\end{aligned}$$

$$\begin{aligned}S &= \sum(1,2,4,7) \\&= \\&=\end{aligned}$$