




Lab 4 Preparation

Lab 4 Parts

■ Part I

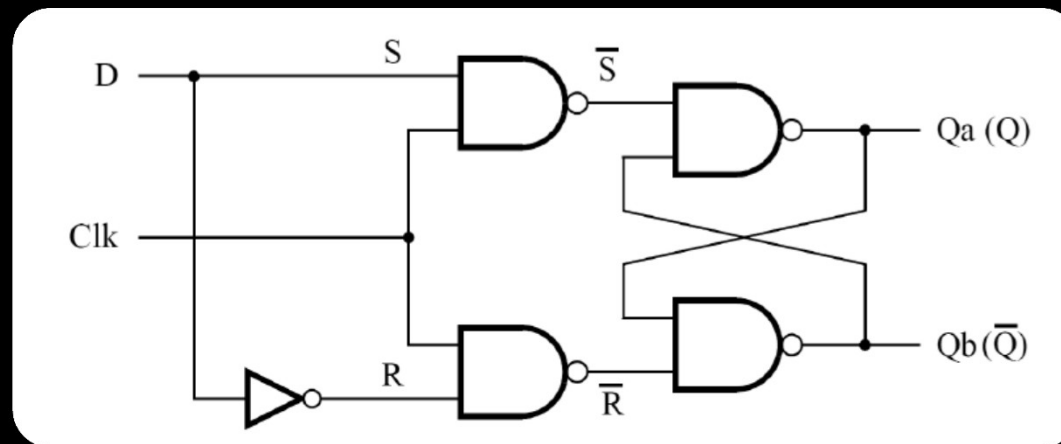
- Create a D latch on the breadboard.
- Same procedure as for Lab 1.



Lab 4 Parts

■ Part II

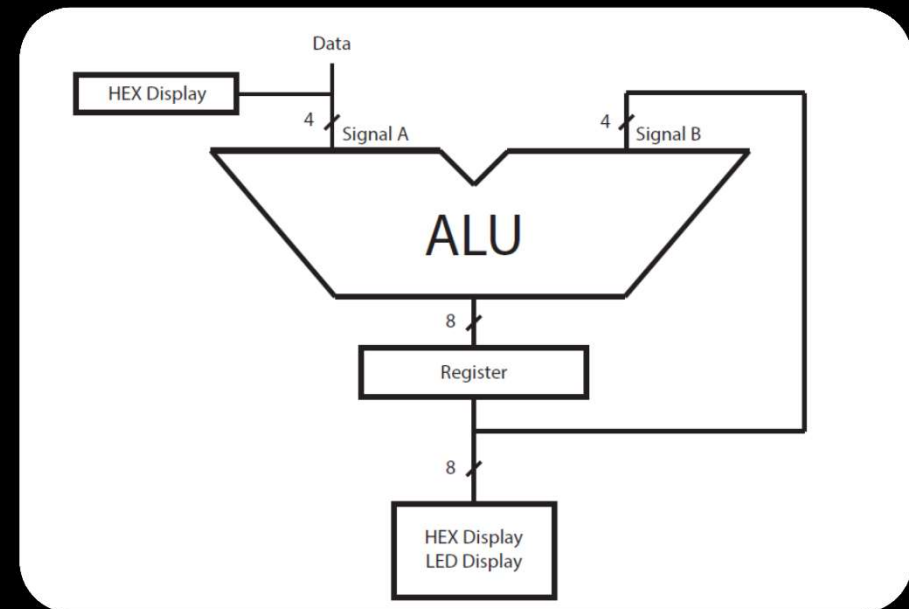- Enhance the ALU from last week:
 - More operations (e.g. multiplication)
 - Memory
- Note: ALU output is now stored in a set of flip-flops called a **register**.
 - 8 flip-flops can be declared together:
`reg [7:0] d;`




Lab 4 Parts

■ Part III

- Make a shifter unit.
- Connect 8 shifter units together.

ShifterBit

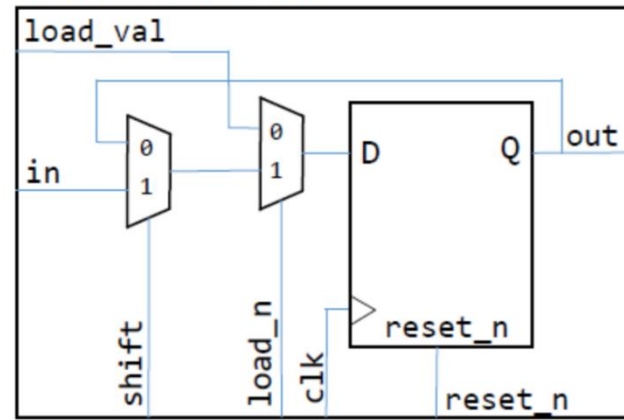

Shift Operations

- **Logic Shift** (left or right)

- Verilog Operators: `<<`, `>>`

- `X >> N`

- Produces a new vector with value of `X` shifted right

- The `N` most-significant bits of the new vector **are filled with zeros**.

- `X << N`

- Produces a new vector with the value of `X` shifted left by `N` bits.

- The `N` least significant bits of the new vector **are filled with zeros**.

```
wire [2:0] a, b;  
wire c;  
assign c = 1'b1;  
assign a = (3'b011 >> 1'b1);  
assign b = a << c;
```

- **Example:**

- `3'b100 >> 2` will produce `3'b001`

- `3'b100 << 2` will produce `3'b000`

Why is Shift Important?

- What is the sum of 01101101 and 01101101?

11011010

← Note what's happening here!

- Try the following:

- 00110 << 1

- 00110 >> 1

$A \ll N$ results in $A * 2^N$

$A \gg N$ results in $A / 2^N$

Logic vs. Arithmetic Shift

- Arithmetic right shifts **replicate the sign bit** instead of using zero to fill in the most-significant bit(s).
 - Needed if dealing with signed numbers (e.g., 2's complement notation)
- **Examples:**
 - Arithmetic Right Shift: 挪完, 填充第一位数字
 - $3'b100 \ggg 2$ will produce $3'b111$
 - Logic Right Shift:
 - $3'b100 \gg 2$ will produce $3'b001$


Sign Extension

- Used in binary arithmetic when we want to increase the # bits used to represent a number while maintaining its sign/value.
- Let's say you want to add these two signed numbers . How would you do that?
 - 0011_1101
 - 0110
 - What if the second number was 1110 instead?

Sign extend this one!

Sign Extension – How?

 - You need to replicate the sign (i.e. the most significant bit in 2's complement form)
 - Replicate 0 for positive numbers
 - Replicate 1 for negative numbers



Implementing D-FF in Verilog

```
module my_dff (clk, reset_n, d, q);  
    input clk;  
    input d;  
    input reset_n;  
    output q;  
    reg q;  
  
    always @(*) begin  
        q <= d;  
    end  
endmodule
```

Need to change this so that q follows d on the positive or negative edge of the clock.

The (\leq) operator is for non-blocking assignments. Use this for sequential circuits.

Implementing D-FF in Verilog

```
module my_dff (clk, reset_n, d, q);  
    input clk;  
    input d;  
    input reset_n;  
    output q;  
    reg q;  
  
    always @ (posedge clk) begin  
        q <= d;  
    end  
endmodule
```

The sensitivity list is now correct. We'll fix the body of the always block next.

Could use **negedge** keyword for negative edge-triggered behaviour.

D Flip-Flop with Reset Signal

- **Reset:** This is how you put your hardware in a known initial state!

```
always @(posedge clk) begin
    if (reset_n == 1'b0)
        q <= 0;
    else
        q <= d;
end
```

if-else used within an always block. Synthesizes to a multiplexer.


Note: Reset is usually **active-low** (meaning it triggers when `reset_n` is low). Here we have an **active-low synchronous reset** signal.

When you test/demo your design

- Synchronous Reset
 - Needs to be 0 @ the active clock edge.
- Be careful with KEYs and active low signals.
 - A KEY on the DE1-SoC board is 0 when pressed.
 - Here's an example
 - Assume I have KEY [0] as my clock and KEY [1] as a signal that is active-low.
 - How can you test for a scenario where KEY [1] is low at the positive edge of your clock?
 - Think about how you will need to press these two keys.

Load register

 - N-bit number \Rightarrow n D-flipflops with same clock signal
- You can load a register's value (all bits at once), by feeding signals into each flip-flop:
 - In this example: a 4-bit **load register**.



Design Guidelines

- Combinational Circuits (e.g., `always @ (*)`)
 - Use blocking assignment statements (`=`)
- Sequential Circuits (e.g., `always @ (posedge clock)`)
 - Use non-blocking assignment statements (`<=`)
- Don't mix assignment types in the same `always` block! 😊
- Order of `always` blocks doesn't matter; neither does the order of `always` blocks and `assign` statements.