




CSC258: Computer Organization



Instructor: Rabia Bakhteri, rabia.bakhteri@mail.toronto.edu

* Original slides by Steve Engels

Breaking down CSC258

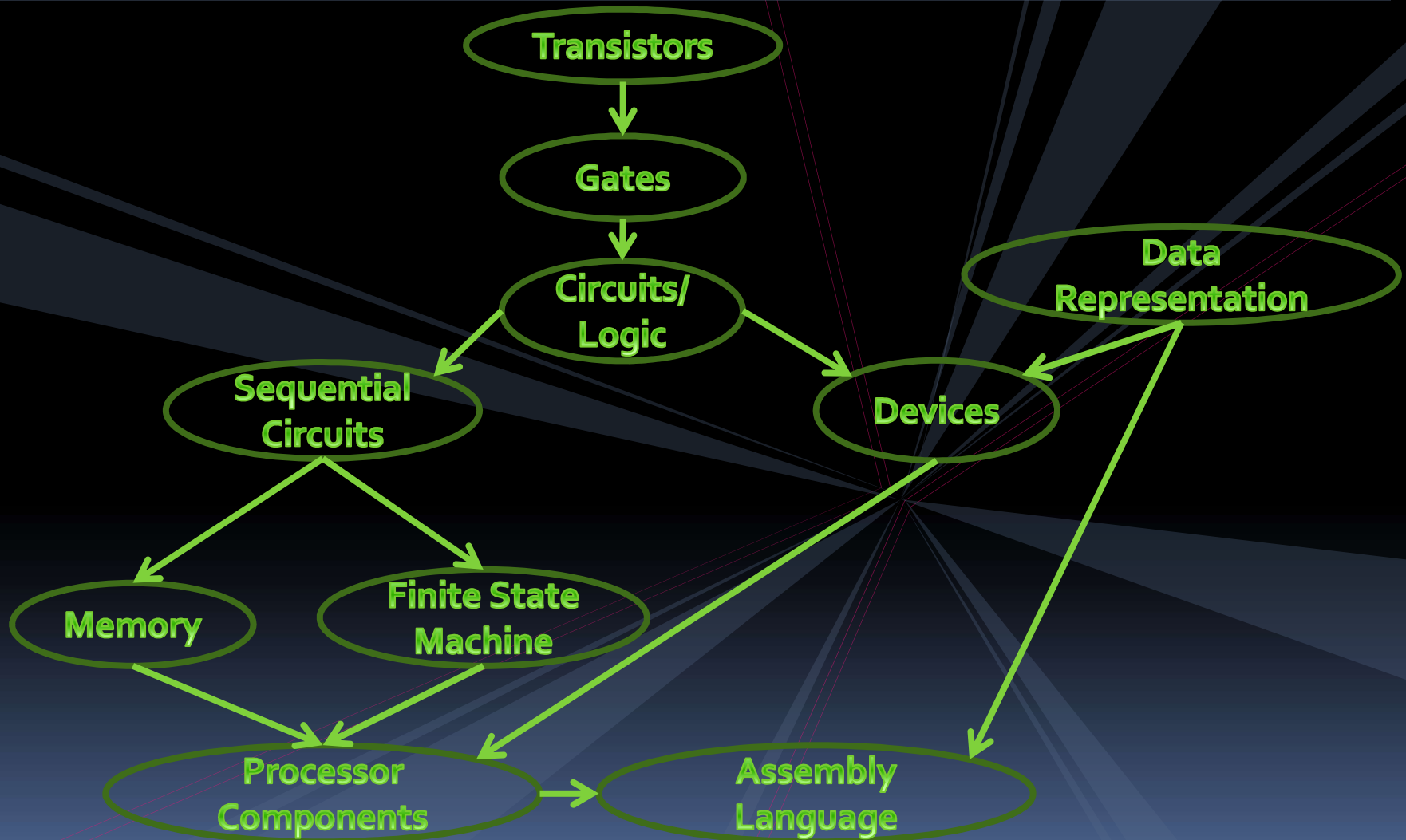

CSC258 Course Details

- **Lectures**

- Lectures cover topics (generally one per week)
- Each week builds on the week before

- **Tutorials**

- 30 minutes topic review (from previous week)
- 30 minutes lab prep (for following week)

- **In-class Quiz (4%)**

- 12 problem sets to be solved in pairs
- To be handed in during class

CSC258 Course Details

- **Labs (28%):**
 - 7 total (4% each)
 - Must complete pre-lab exercises ahead of time (1%) and demonstrate completed lab tasks to TAs in the lab rooms (BA3145, BA3155, BA3165).
 - Must work in pairs, in your assigned room.
 - Your partner and your lab station are yours for the duration of all 7 labs.
 - No eating or drinking allowed in the lab rooms.

CSC258 Course Details


- **Project (10%):**
 - Project proposal (1%)
 - 3 milestone demos (3% each)
 - Goal: Large, cool digital creation.
- **Exams:**
 - **Midterm (18%)** – June 26th, 6pm-8pm
 - Email me ASAP if you have conflicts.
 - **Final exam (40%)**
 - Must get 40% to pass the course.



Finally, two common questions

What is the point of this
course?

Why are you making
me take this?



“Why are you making me take this?”

- CSC258 isn't needed if you're just a causal technology user.
 - You can still drive a car, even if you don't understand how the engine works.




“Why are you making me take this?”

- Computer science majors aren't casual technology users.
 - At the very least, you'll need to know how the programs you write are affected by hardware.
 - Processor knowledge is needed for OS courses.
 - Assembly language is needed for low-level tasks like compilers.



“What is the point of this course?”

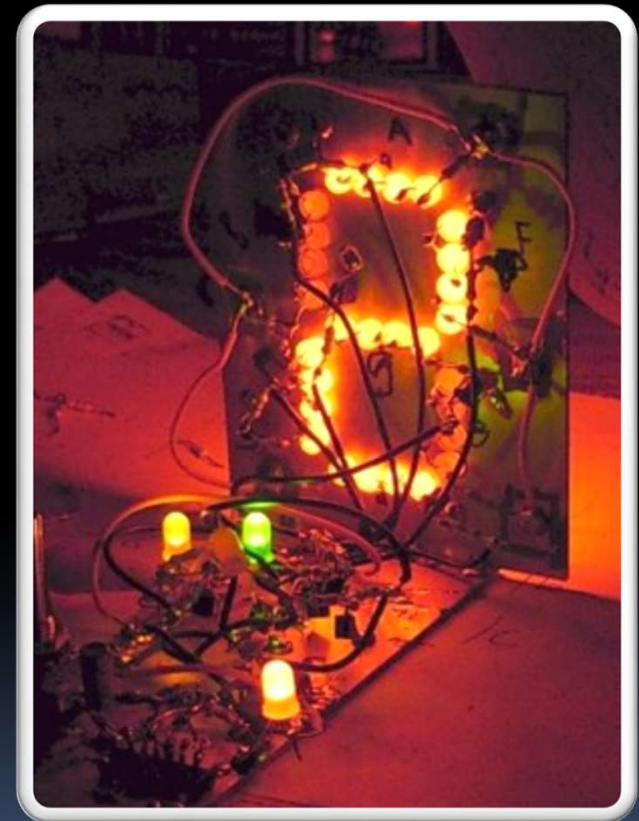- Course outcomes:
 - Understand the underlying architecture of computer systems.
 - Learn how to use this architecture to store data and create behaviour.
 - Use the principles of hardware design to create digital logic solutions to given problems.



“What is the point of this course?”

- Our course goals:
 - Make you a better computer scientist.
 - Expose you to new programming paradigms.
 - Give deeper insights into past/current courses.
 - Help prepare you for future courses.
- How we do this:
 - Show you how your computer works.
 - Start from electricity, end with assembly.

Let the learning begin



A few questions to start

- How much do you actually understand about your computer and the programs you run?
- For instance:
 1. When you set a variable to "false" or "true", how are these boolean values stored?
 2. Why is there a maximum value for an `int`?
 3. Is it cheaper to do an addition operation or a multiplication?
 4. How do boolean operations like "and", "or" and "not" work?
 5. What happens when you press `Ctrl-Alt-Delete`?
 6. What happens when you compile a Java or C program?
 7. What causes a blue screen error on your computer?

CSC258 has the answers

- Computers are physical things, therefore they have certain behaviours and limitations:
 - Data values are finite.
 - All data is stored as ones and zeroes at some level.
 - Many high-level operations depend on low-level ones.
- The way computers are today take their origins from how computers were created in the past.



Example #1: Booleans

- How are boolean values stored?
- Example: `if` statements:

```
if x:  
    print 'Hello World'  
    # what values can x have  
    # that make this happen?
```

- What if `x` is a boolean?
- What if `x` is an int?
- What if `x` is a string?

} All comes down to
hardware in the end!

Example #2: Integers

- How are `int` values stored?

- Again, as ones and zeroes.

Decimal → 1234 → 0011000000111001 Binary

- How many values can integers have?

- This can vary based on language and architecture, but **generally integers have 2^{32} different values.**



- Signed integers: range from -2^{31} to $2^{31}-1$

- Unsigned integers: range from 0 to $2^{32}-1$

- Different ranges for `long`, `short` and `byte`.

What does all this involve?

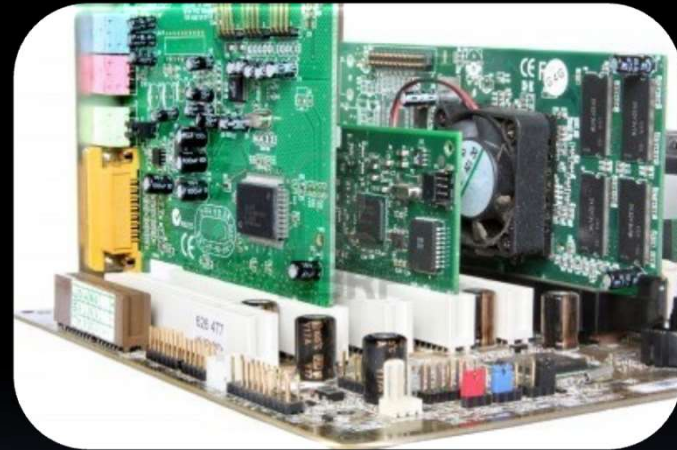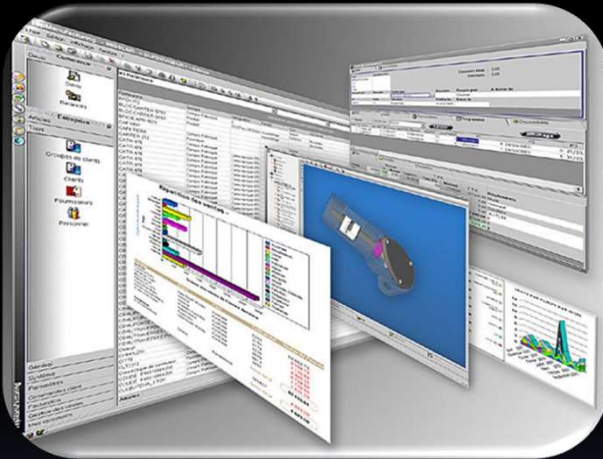- Computers do on the hardware level what programs do on the software level.



- In CSC258, designing circuits follows many of the same ideas behind creating boolean logic in Python or Java.



Programming parallels

Python/Java


- Boolean variables
- Boolean operations (and, or, not, etc)
- Integers, doubles, chars
- Addition, subtraction, multiplication
- Storing values
- Executing instructions

Computer hardware

- High and low wire values
- Logic gates (AND, OR, NOT, etc)
- Registers
- Adder circuits, multiplier circuits
- Memory
- Processors



Things you already know

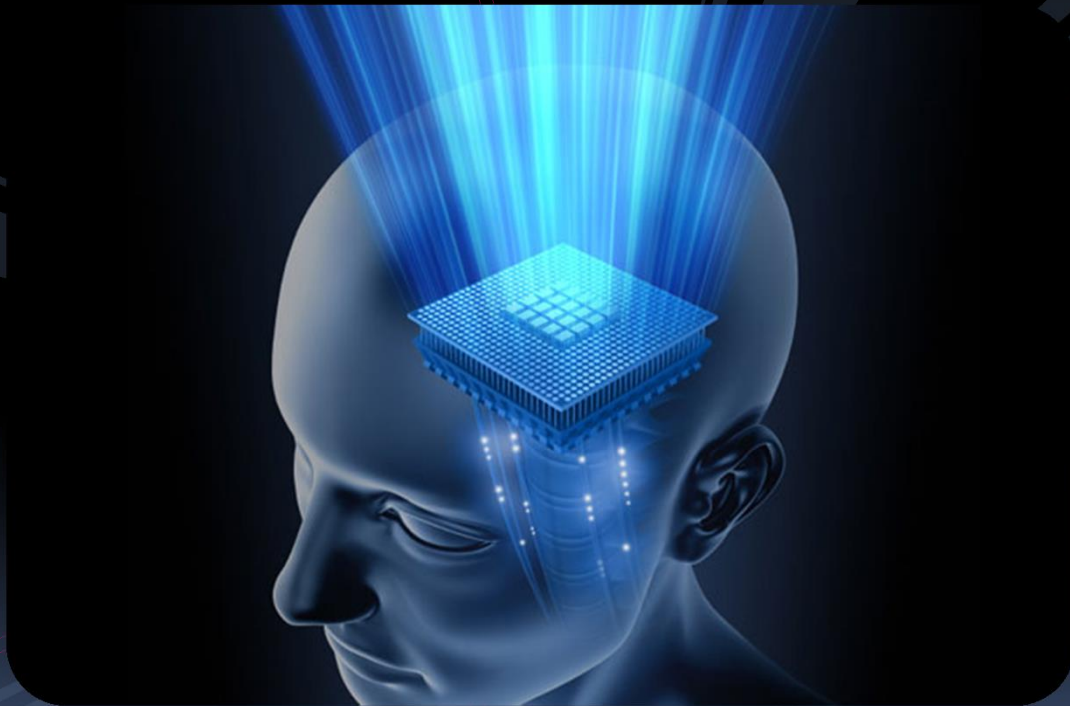

Programming from CSC148


- You need to have basic coding literacy.
- *However...*
 - For CSC258, be prepared to let that all go.
 - Verilog → specification language
 - Assembly → low-level programming
 - Trying to connect these languages to CSC148 will only hold you back.
 - Embrace new ways of thinking.

Logic from CSC165

- Thanks to CSC165, you're already familiar with the first piece of CSC258: basics of **logic gates**.
- CSC165 example: Create an expression that is true if the variables A and B are true, or C and D are true.





$$G = A \ \& \ B \ | \ C \ \& \ D$$

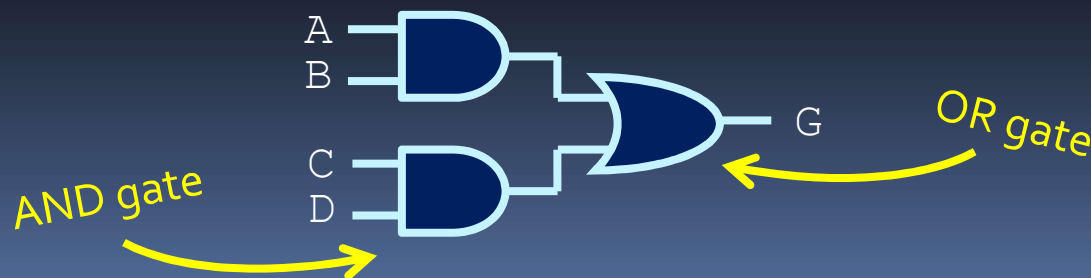- CSC258 example: Create a circuit that turns on if inputs A and B are on, or inputs C and D are on:





From CSC165 to logic gates

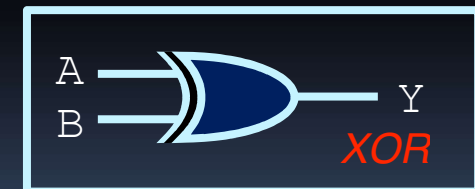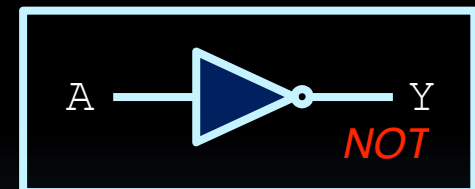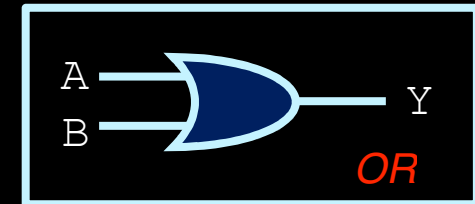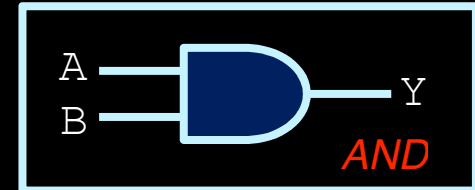- We start with CSC165 basics to create simple circuits based on logical expressions, and expand from there to create bigger and more complicated systems.
- Each of these fundamental logical expressions is represented by a piece of hardware called a **gate**, that turns an output signal on based on which input signals are on.





AND Gates

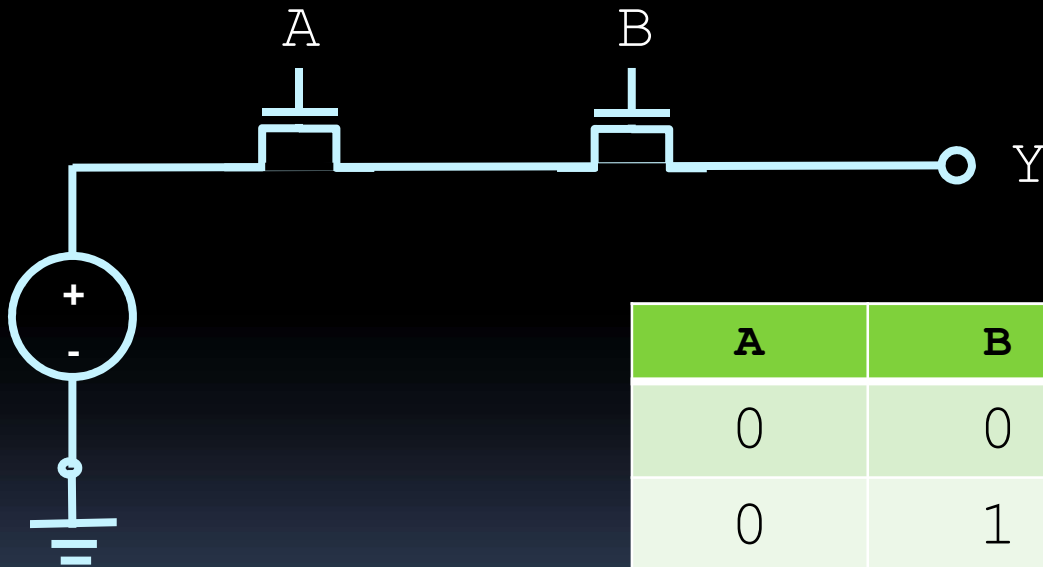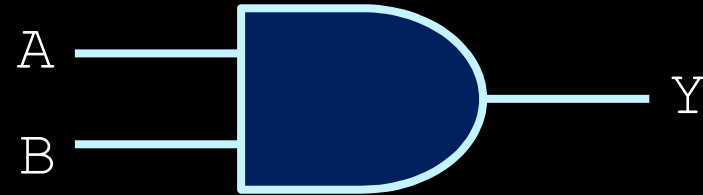



A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

OR Gates

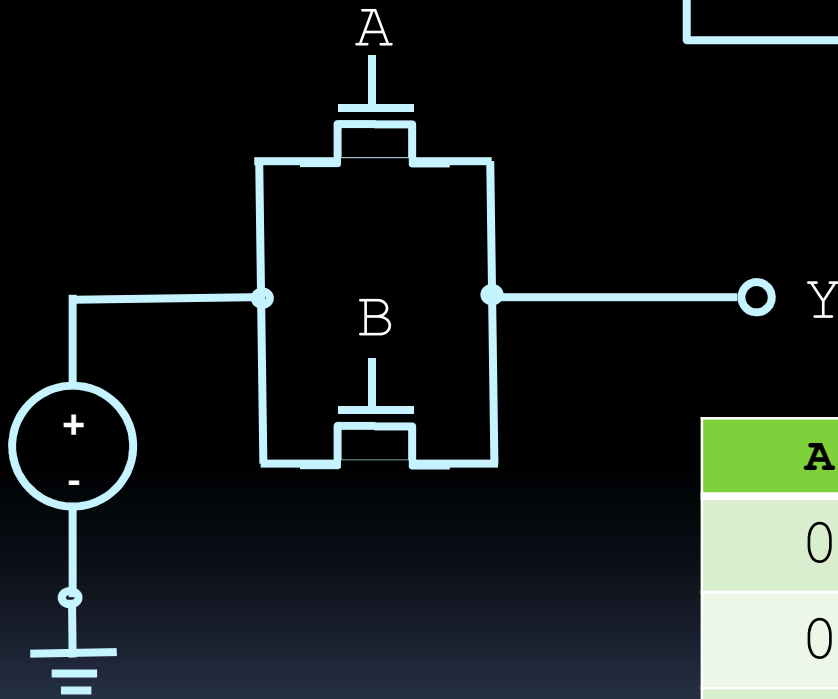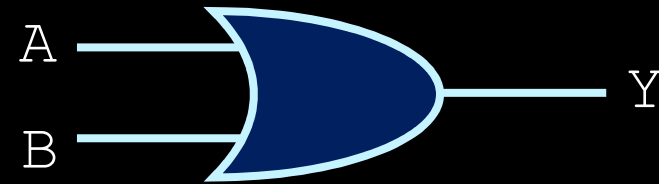



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

NOT Gates

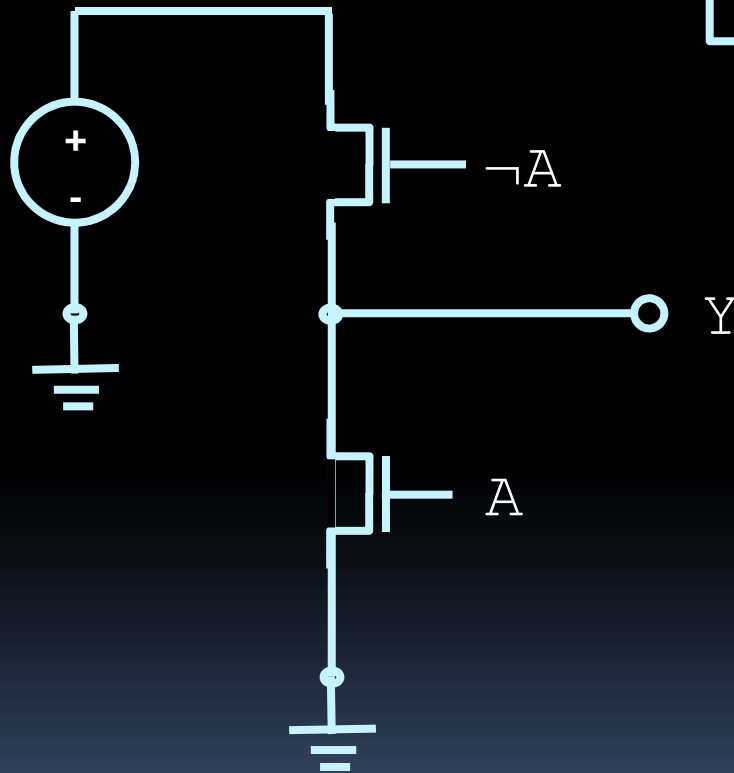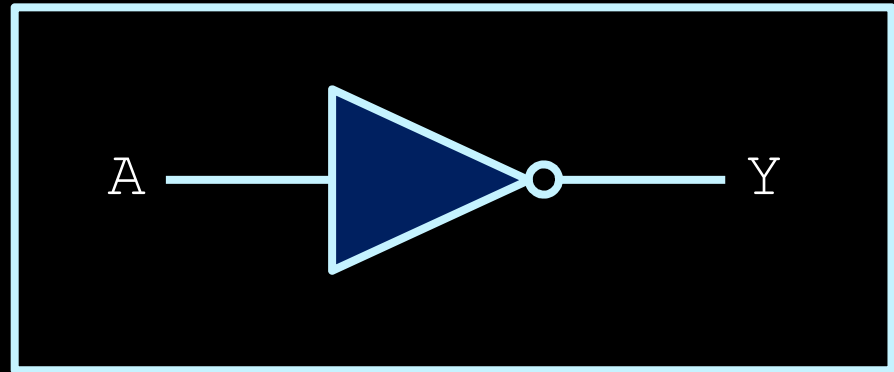

A	Y
0	1
1	0

XOR Gates

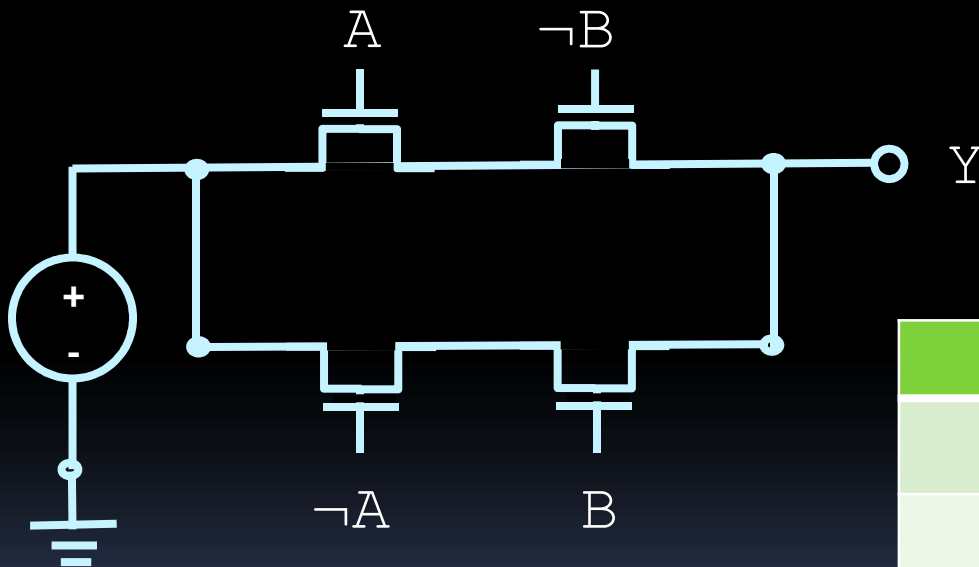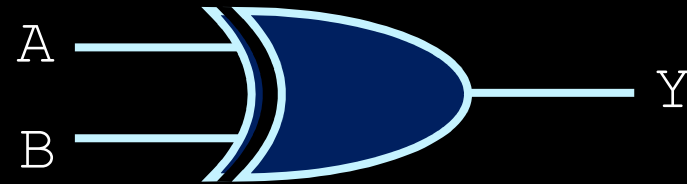



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Bill Gates



- ...ha ha...moving on....



not and NAND Gates

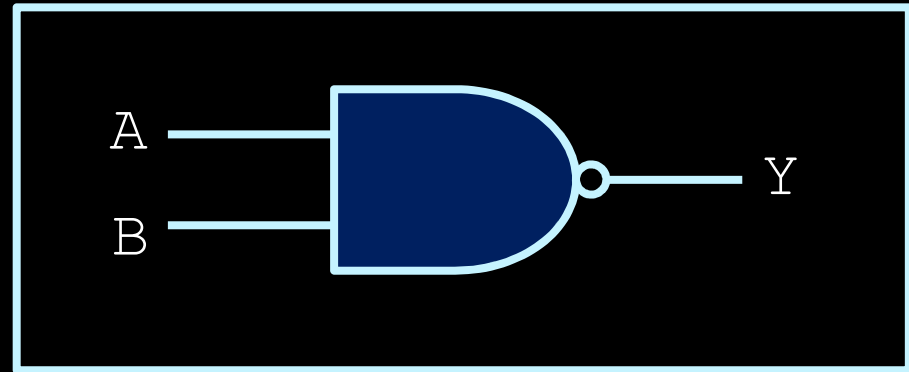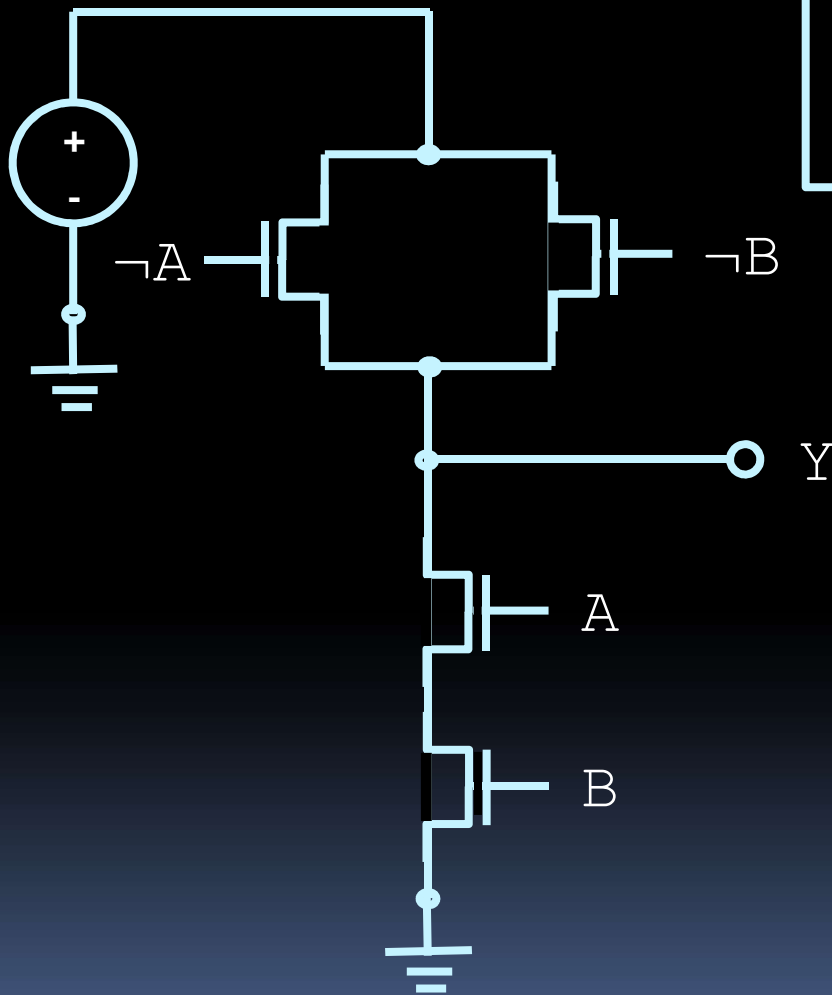

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



not or

NOR Gates

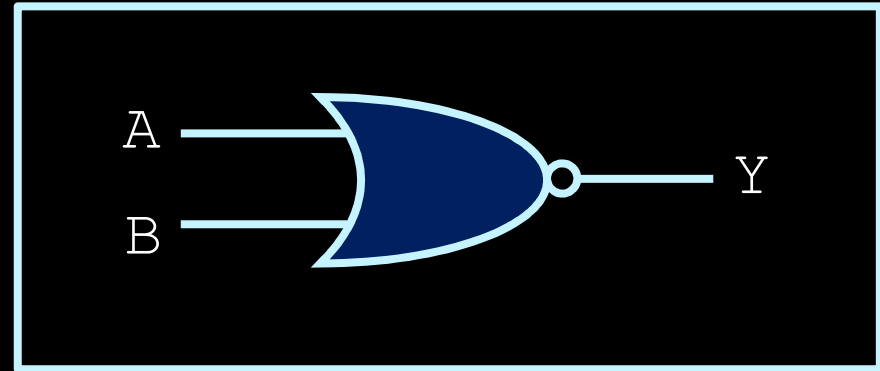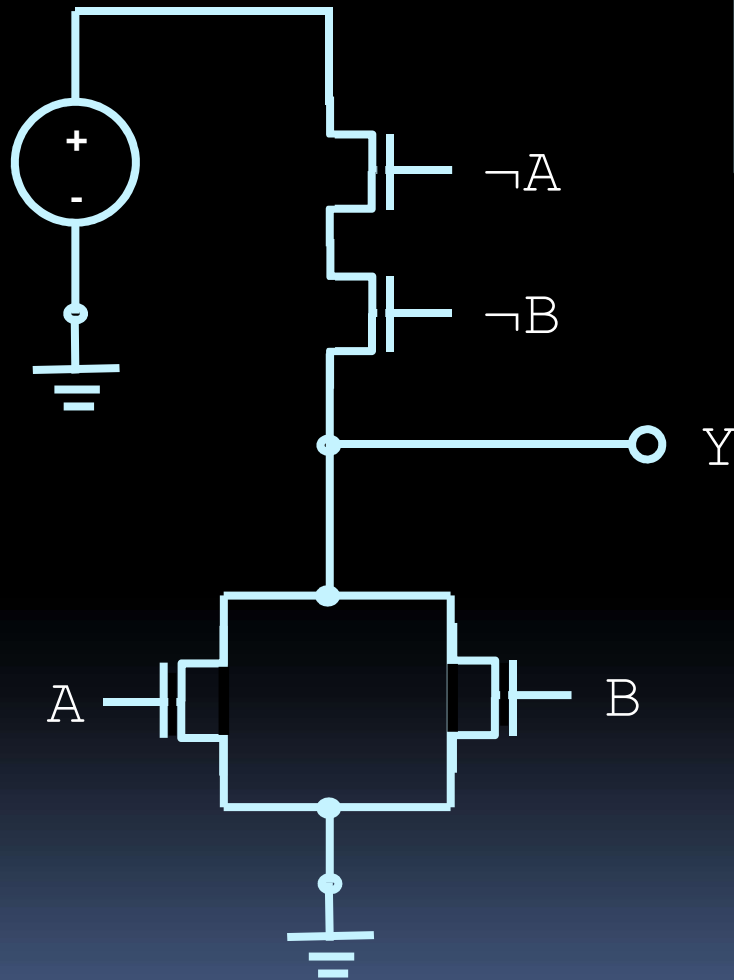

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0



Buffer

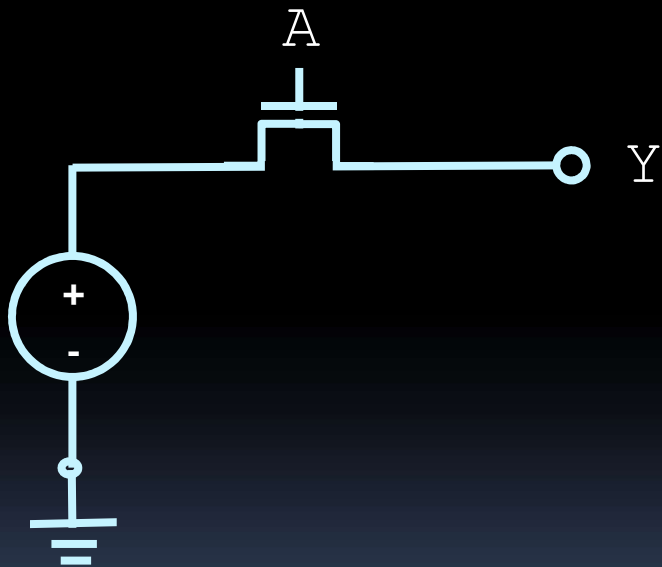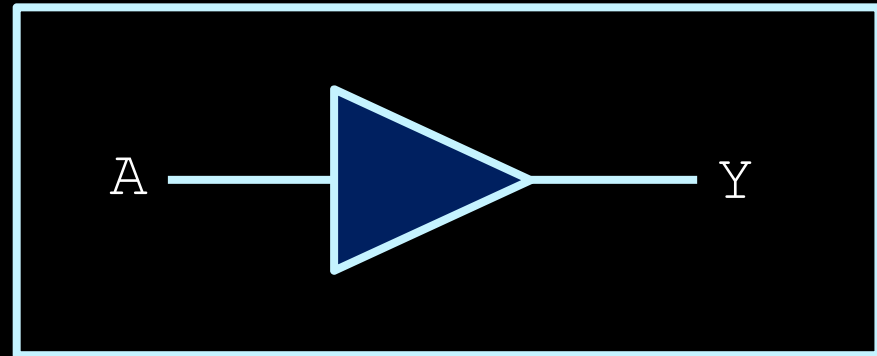

A	Y
0	0
1	1

From gates to CSC165

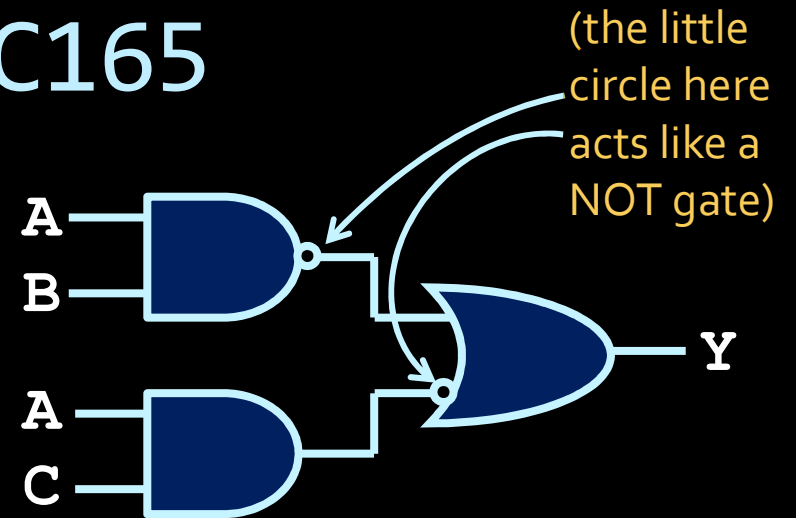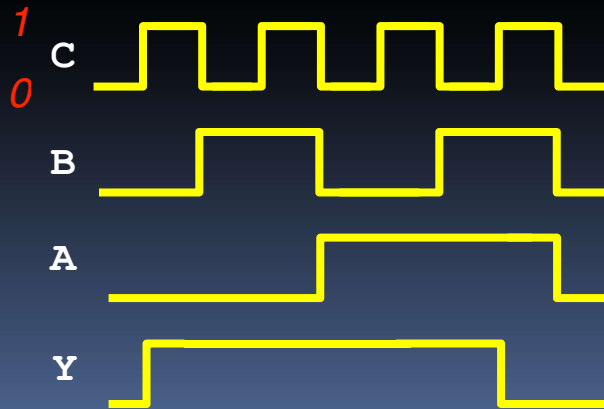- Given a logic problem or circuit, can you make a truth table to describe its behavior (as in CSC165)?
 - Sometimes illustrated using a **waveform**.




A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


From expressions to circuits

- Creating and expressing circuit logic is similar to working with boolean logic in Python, C or Java:
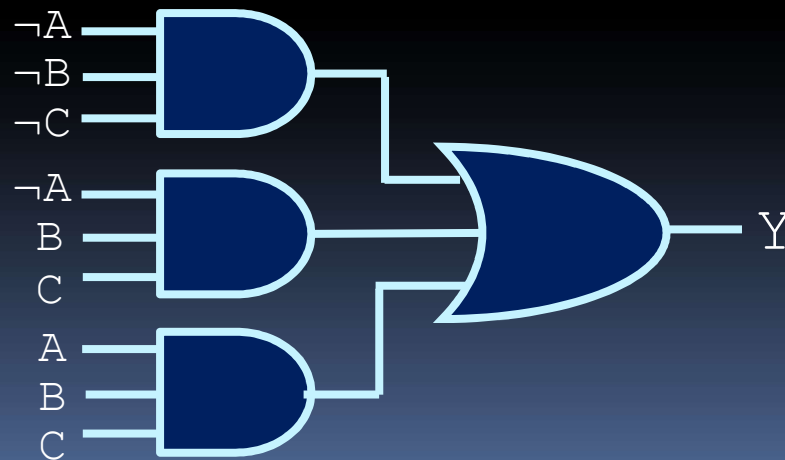
```
Y = (!A and !B and !C) or (!A and  
    B and C) or (A and B and C)
```



Things you might not know yet

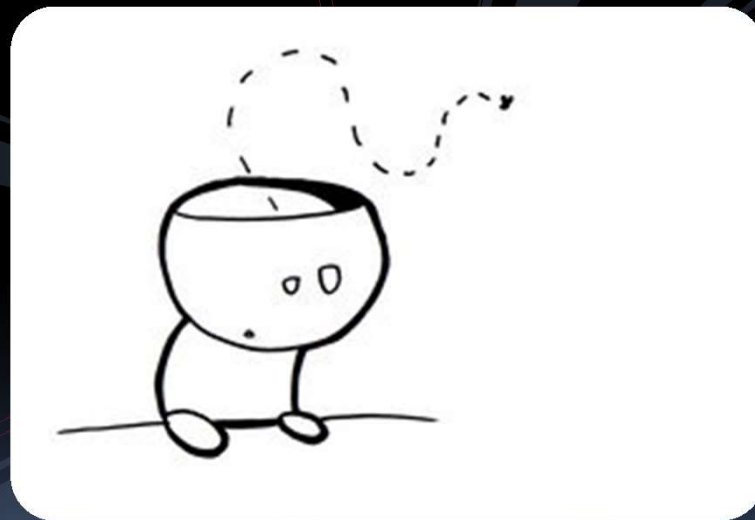



Thinking in hardware

- Although CSC258 has elements that are similar to other courses, it is very different in significant ways.
 - Unlike other software courses, CSC258 is not about creating programs and algorithms, but rather devices and machines.
 - Very important concept to grasp early in this course!
 - For instance: We need to understand what certain terms mean in the context of hardware.




“True” and “False” in CSC258

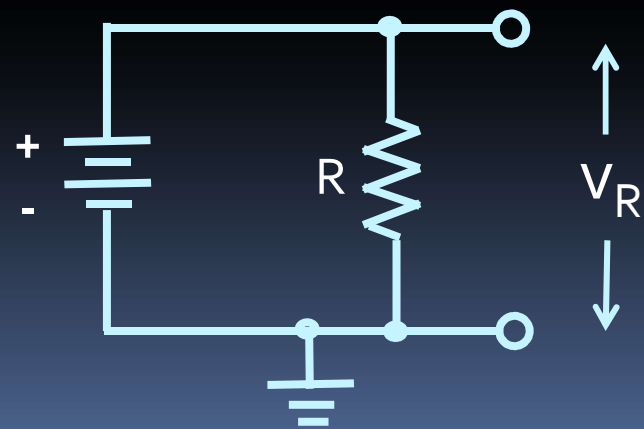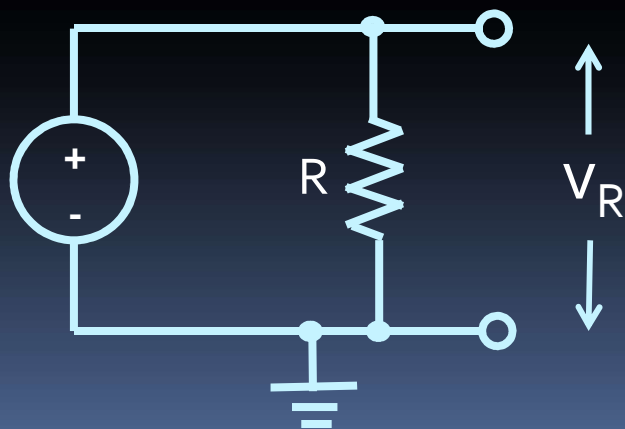- If a circuit performs a logical operation, how does it represent “true” and “false”?
 - In hardware, these boolean values are represented as **electrical voltage values** on a wire:
 - “False” (aka zero): little to no voltage at that point.
 - “True” (aka one): typically a voltage difference of 5 volts, relative to the ground.



Behind gates

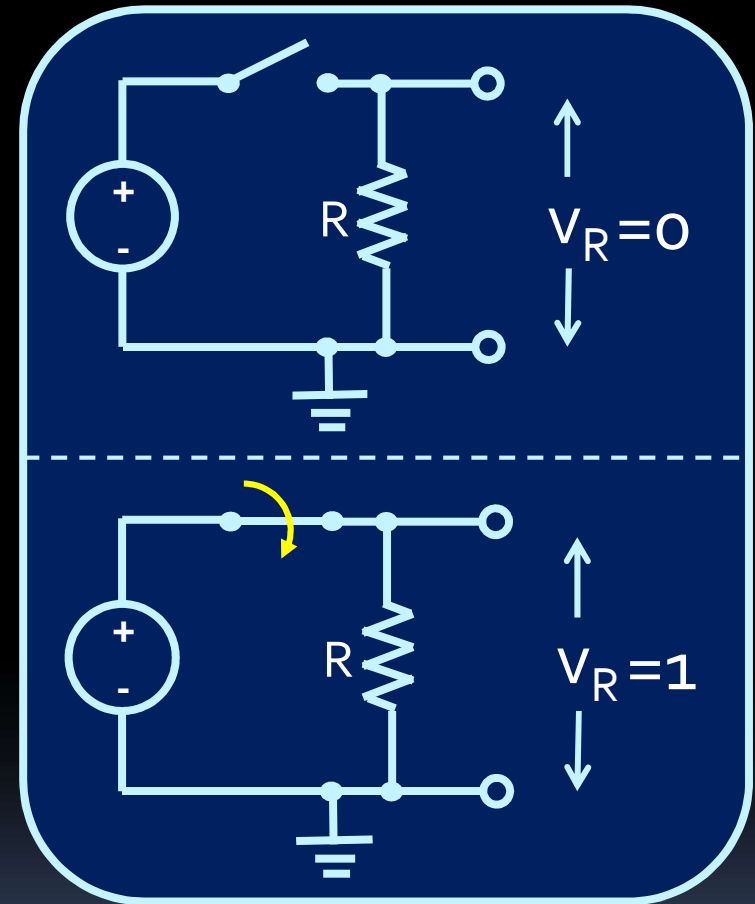
- For electricians, **switches** are physical devices for manually closing a circuit.
- **Gates** are like switches, which control whether an output wire will have a high value (5V) or a low value (0V)
 - Unlike physical switches, gates are semi-conductor devices that take electrical inputs to close the circuit.



Expressions = circuits

- CSC258 tasks assume that we have input signals can be turned on (one) or off (zero), and we need outputs that combine these signals together.
 - Example #1: If the Ctrl, Alt and Delete buttons are being pressed, restart the computer.
 - Example #2: If a train is approaching the platform, only turn on the green signal light if the track is clear and the previous train is a certain distance away.
- Every electronic device uses gates to combine input signals to create these output signals.
 - Very similar to CSC165 problems, but in hardware.

Example: Ctrl-Alt-Delete

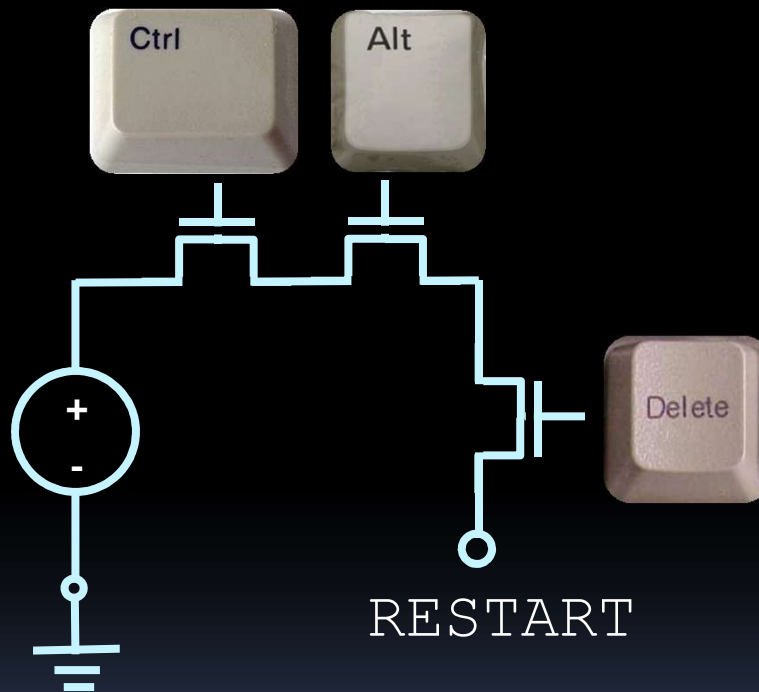


Ctrl	Alt	Del	RESTART
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

What we ask you to do (e.g. labs)

- Given a truth table or circuit description, determine the circuit that creates it.
- Look at the conditions that cause high output signals.
- Express the high conditions as a boolean statement, then convert this to gates.

A	B	C	MOVE
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

The course at a glance

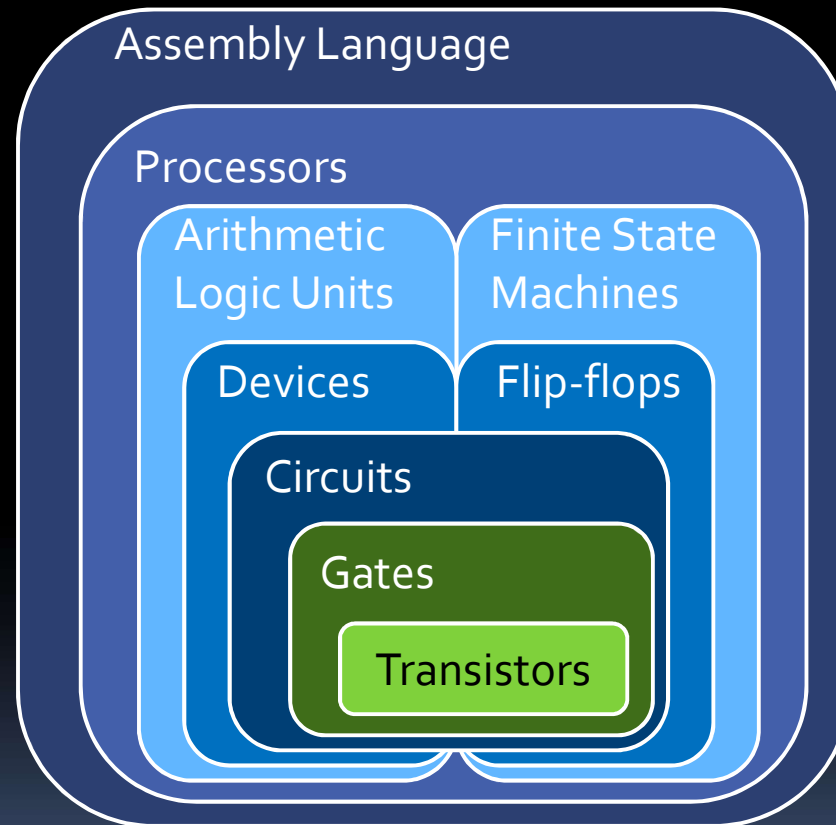

Starting from the bottom

- Gates can combine values together like logical operators in C or Java.
- But how do gates work?
 - First, we need to understand electricity.
 - Then, we need to understand **transistors**.

